

1. Introductions

1.1. Basic Function and Design Goals

 


Fig. 1.1 A typical architecture of radio receiver

1.1.1. Basis Function

- Provide gain to minimize noise contributed by subsequent blocks
- Contribute as low noise as possible
- Provide high linearity
- Provide 50 ohm input impedance
- Low power dissipation

1.1.2. Design Goals

- Simultaneous Noise and Input Matching
- Any given amount of power dissipation

2. Fundamental of Low Noise Amplifier

2.1. Noise Figure and Noise Factor

The most popular basis definition of noise figure is given by Friis

$$NF = 10 \log \left(\frac{SNR_{in}}{SNR_{out}} \right) = 10 \log (F) \quad (2.1)$$

where SNR_{in} and SNR_{out} are the signal-to-noise ratios measured at the input and output

NF measures how much the SNR degrades as the signal passes through a system

**If a system has no noise, then $SNR_{in} = SNR_{out}$
 \rightarrow NF of noiseless system is equal to 0 dB**

2.2. Power Gain

 


Fig. 2.1 NF of the cascade system

$$NF_{total} = NF_1 + \frac{NF_2 - 1}{A_1} + \dots + \frac{NF_n - 1}{A_1 \cdot A_2 \dots A_n} \quad (2.2)$$

- **NF of overall system is dominated by first stage**
- **\rightarrow LNA need to have high gain to suppress the noise contributed by later stages**
- **However be careful when design high gain because it easily becomes oscillator**

2.3. Linearity

- ✓ LNA must remain linear even when strong signals are being received
- ✓ The nonlinear can be characterized by 1 dB compression point (P-1dB) or input referred third order intercept point (IIP3)
 - P-1dB is defined as the input power at which the output power gain drops by 1 dB
 - IIP3 is defined as the point at which extrapolated fundamental response and the extrapolated third order intermodulation line intersect

$$IIP3 = \frac{P_{out} - P_{out,IM3}}{2} + P_{in} \qquad \frac{A_{P-1dB}}{A_{IIP3}} \approx -9.6 \text{ dB}$$

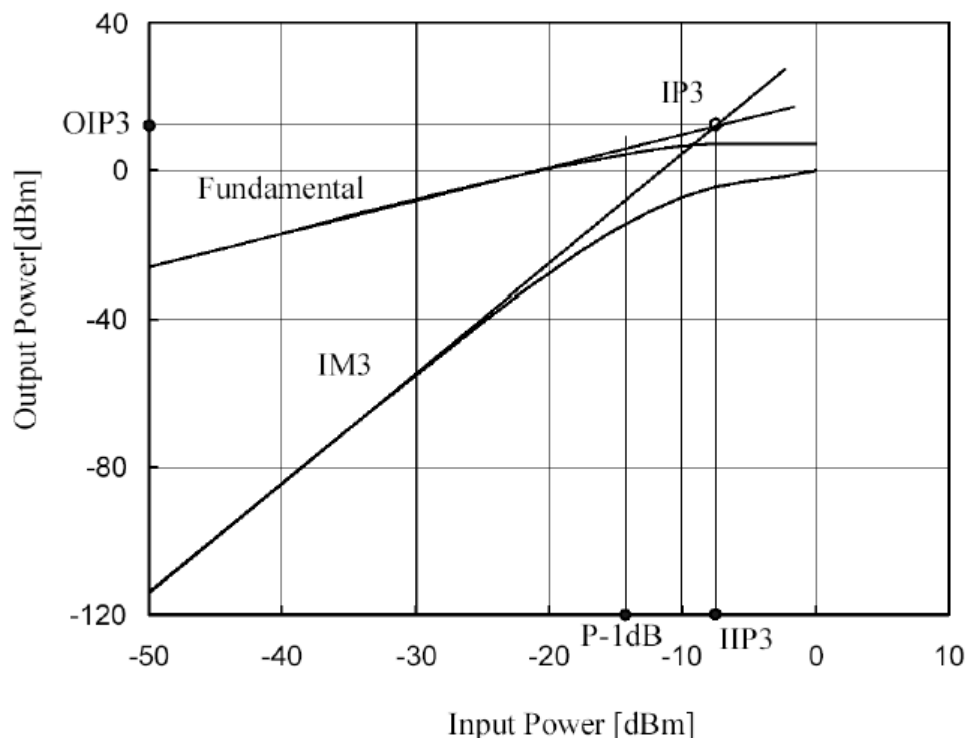


Fig. 2.2 A Plot of IIP3

3. Low Noise Amplifier Design Techniques

3.1. Classical Noise Optimization Technique


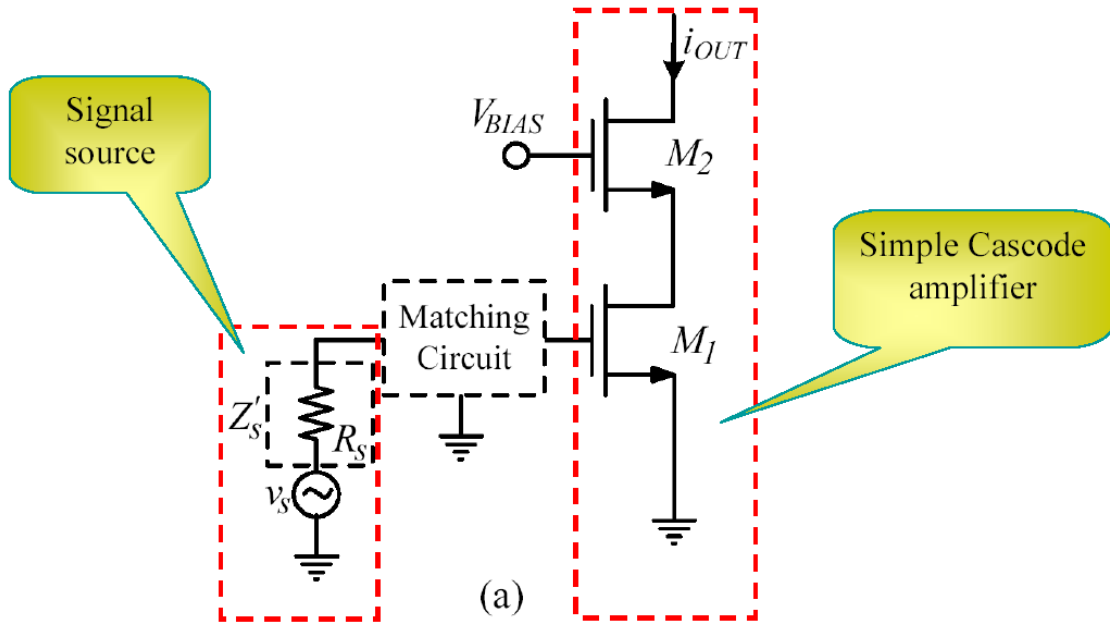


Fig. 3.1. (a) The schematic of cascode topology apply to adopt CNM technique
(b) Small signal equivalent circuit

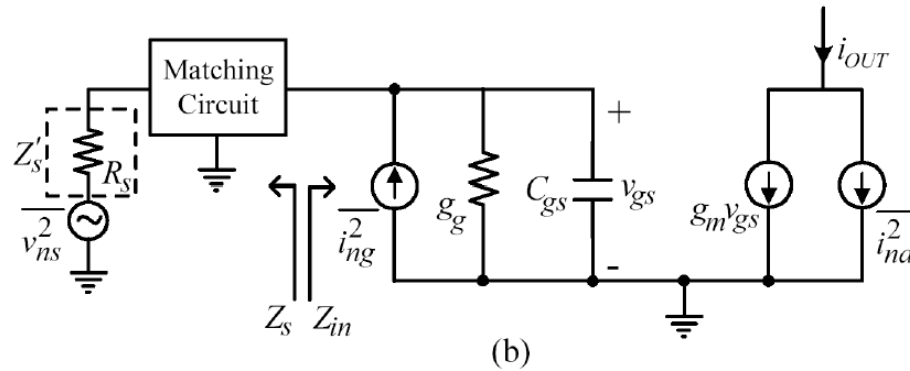

✓ The mean-square channel thermal noise current

$$\overline{i_{nd}^2} = 4kT\gamma g_{d0}\Delta f \quad (3.1)$$

✓ The mean-square gate-induced noise current

$$\overline{i_{ng}^2} = 4kT\delta g_g\Delta f \quad (3.2)$$

$$g_g = \frac{\omega^2 C_{gs}^2}{5 g_{d0}} \quad (3.3)$$

$$c \equiv \frac{\overline{i_{ng} \cdot i_{nd}^*}}{\sqrt{\overline{i_{ng}^2}} \cdot \sqrt{\overline{i_{nd}^2}}} \quad (3.4)$$

- g_{d0} is drain-source conductance at zero drain-source voltage
- k the Boltzmann constant
- T absolute temperature
- C_{gs} drain-source capacitor
- γ has value of 1 at $V_{DS}=0$ and 2/3 at saturation mode
- γ increases to more than 2 in short channel device
- $\delta=4/3$ in long-channel and increases in short-channel devices
- c is correlation coefficient and equal to $j0.395$

The noise parameters are given by [3]

✓ **Noise Resistance**

$$R_n^o = \frac{\gamma}{\alpha} \cdot \frac{1}{g_m} a \quad (3.5)$$

- For small $R_n \rightarrow$ increase transistor size and drain current

✓ **Minimum Noise Figure**

$$F_{min}^o = 1 + \frac{2}{\sqrt{5}} \frac{\omega}{\omega_T} \sqrt{\gamma \delta (1 - |c|^2)} \quad (3.6)$$

- Strong function of ω_T and ω
- Technology scaling $\rightarrow \omega_T \uparrow$, γ , σ , and $c \downarrow \rightarrow F_{min} \downarrow$

✓ **Optimum Noise Admittance**

$$Y_{opt}^o = \alpha \omega C_{gs} \sqrt{\frac{\delta}{5\gamma} (1 - |c|^2)} - sC_{gs} \left(1 + \alpha |c| \sqrt{\frac{\delta}{5\gamma}} \right) \quad (3.7)$$

$$\alpha \equiv g_m / g_{do}$$

- **Composed of real and imaginary value**
- **Increase with Tr. size and frequency**
- **Imaginary part: inductive but capacitive in frequency behavior**
 → allow only narrowband matching

✓ **From Fig. (b), the input admittance is**

$$Y_{in}^o = j\omega C_{gs} \quad (3.8)$$

$$\longrightarrow Y_{in}^{o*} = -j\omega C_{gs}$$

$$\boxed{Y_{opt}^o = \alpha \omega C_{gs} \sqrt{\frac{\delta}{5\gamma} (1 - |c|^2)} - sC_{gs} \left(1 + \alpha |c| \sqrt{\frac{\delta}{5\gamma}} \right)}$$

- Y_{in}^{o*} **Imaginary component only**
- **Inherent mismatch between Y_{in}^{o*} and Y_{opt}^o**
 → no simultaneous noise and input matching

- ✓ Design for minimum NF by presenting Z_{opt} to the given transistor
- ✓ Typically require matching circuit
- ✓ Can achieve $NF = F_{min}$ of input transistor
- ✓ Inherent mismatch between Z_{opt} and $Z_{in}^* \rightarrow$ input mismatch
- ✓ Often compromise gain and noise performance

3.2. Simultaneous Noise and Input Matching Technique

3.2.1. Circuits Topology


 


Fig. 3.2. (a) The schematic of cascode topology apply to adopt SNIM technique
(b) Small signal equivalent circuit

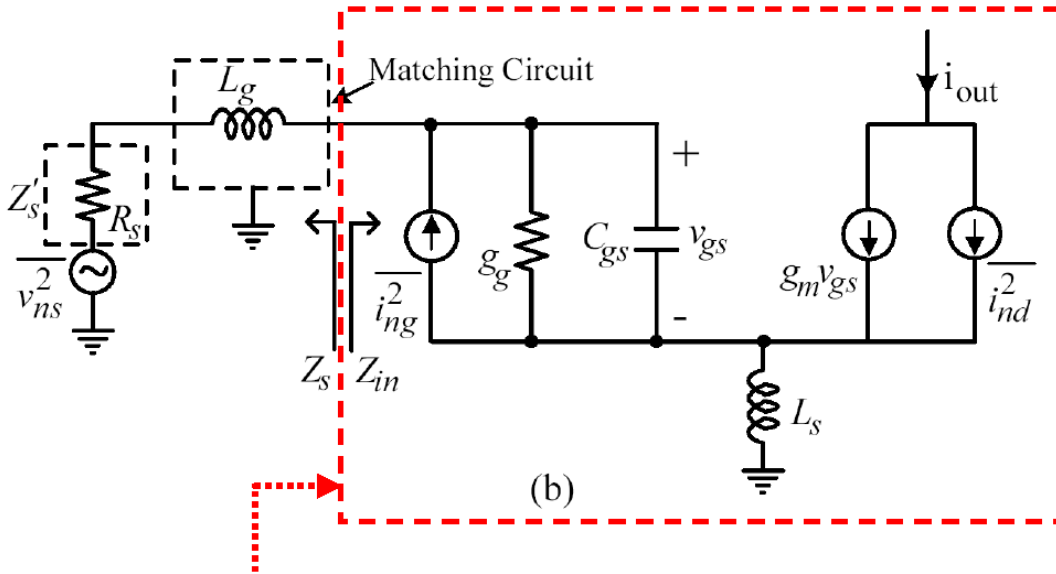Assume inductors are lossless, and matching circuit is implemented by a series inductor, but results are valid for arbitrary matching circuits.



Obtain noise parameters by applying KCL/KVL

3.2.2. Noise Parameters

The noise parameters are given by [Appendix]

✓ **Noise Figure Expression**

$$F = 1 + \frac{1}{g_m^2 R_s} \cdot \left\{ \gamma g_{d0} \cdot \left\{ \begin{aligned} &\left[1 + s^2 C_{gs} (L_g + L_s) \left(1 + |c| \alpha \sqrt{\frac{\delta}{5\gamma}} \right) \right]^2 \\ &- (s C_{gs} R_s)^2 \left(1 + |c| \alpha \sqrt{\frac{\delta}{5\gamma}} \right)^2 \\ &-\frac{\alpha \delta}{5} (1 - |c|^2) g_m (s C_{gs})^2 (R_s^2 - s L_g^2) \end{aligned} \right\} \right\} \quad (3.9)$$

✓ **Noise Resistance**

$$R_n = R_n^o = \frac{\gamma}{\alpha} \cdot \frac{1}{g_m} \quad (3.10)$$

✓ **Minimum Noise Figure**

$$F_{min} = F_{min}^o = 1 + \frac{2}{\sqrt{5}} \frac{\omega}{\omega_T} \sqrt{\gamma \delta (1 - |c|^2)} \quad (3.11)$$



Same as that of the
CNM technique

✓ **Optimum Noise Impedance**

$$Z_{opt} = Z_{opt}^o - sL_s \quad (3.12)$$

$$Z_{opt}^o = 1/Y_{opt}^o = \frac{\alpha \sqrt{\frac{\delta}{5\gamma(1-|c|^2)}} + j \left(1 + \alpha |c| \sqrt{\frac{\delta}{5\gamma}} \right)}{\omega C_{gs} \left\{ \frac{\alpha^2 \delta}{5\gamma(1-|c|^2)} + \left(1 + \alpha |c| \sqrt{\frac{\delta}{5\gamma}} \right)^2 \right\}} \quad (3.13)$$

- $L_s \rightarrow$ No effect on $\text{Re}[Z_{opt}]$, but cancel out $\text{Im}[Z_{opt}]$

✓ The input impedance Z_{in} can be expressed as

$$Z_{in} = sL_s + \frac{1}{sC_{gs}} + \frac{g_m L_s}{C_{gs}} = sL_s + \frac{1}{sC_{gs}} + \omega_T L_s \quad (3.14)$$

✓ From Eq. (13), Eq. (12) can be re-expressed as

$$Z_{opt} = \text{Re} \left[Z_{opt}^o \right] - m \frac{1}{sC_{gs}} - sL_s \quad (3.15)$$

- $m = 0.6$ for the typical device parameters of long channel
- $m \approx 1$ with the advantage technologies (0.25 um CMOS, $c \approx 0.5$, $\alpha < 1$ [39])

→ L_s help to bring the $Z_{opt} \approx Z_{in}^*$ while causing no degradation in F_{min} and R_n

- ✓ **The condition that allows simultaneous noise and input matching is**

$$Z_{opt} = Z_{in}^* \quad (3.16)$$

✓ **Or**

$$\text{Re}[Z_{opt}] = \text{Re}[Z_s] \quad (3.17)$$

$$\text{Im}[Z_{opt}] = \text{Im}[Z_s] \quad (3.18)$$

$$\text{Im}[Z_{in}] = -\text{Im}[Z_s] \quad (3.19)$$

$$\text{Re}[Z_{in}] = \text{Re}[Z_s] \quad (3.20)$$

Step-by-Step Design process

- 1) For a given Z_s ,
- 2) Choose C_{gs} (or W) that satisfies $\text{Re}[Z_{opt}] = \text{Re}[Z_s]$
- 3) Choose L_s that satisfies $\text{Im}[Z_{opt}] = \text{Im}[Z_s]$
- 4) Choose V_{GS} that satisfies $\text{Re}[Z_{in}] = \text{Re}[Z_s]$
- 5) Given L_s satisfies $\text{Im}[Z_{in}^*] \approx \text{Im}[Z_{opt}]$ automatically
- 6) $\rightarrow Z_{opt} = Z_{in}^* = Z_s$
- 7) If Z_s is not equal to Z_s' , add matching circuit
- 8) \rightarrow Noise/input matched simultaneously for given Z_s


3.2.3. Design Process

The following steps describe the procedure how to design LNA based on cascode topology. Since there is no guideline how to choose the cascode transistor to obtain the best performances such as NF, Power gain, and Linearity. Assume that the size of cascode transistor is chosen to be equal to the input transistor. And also assume that the gate bias of the cascode transistor is V_{dd} .

1) Choose V_{GS}

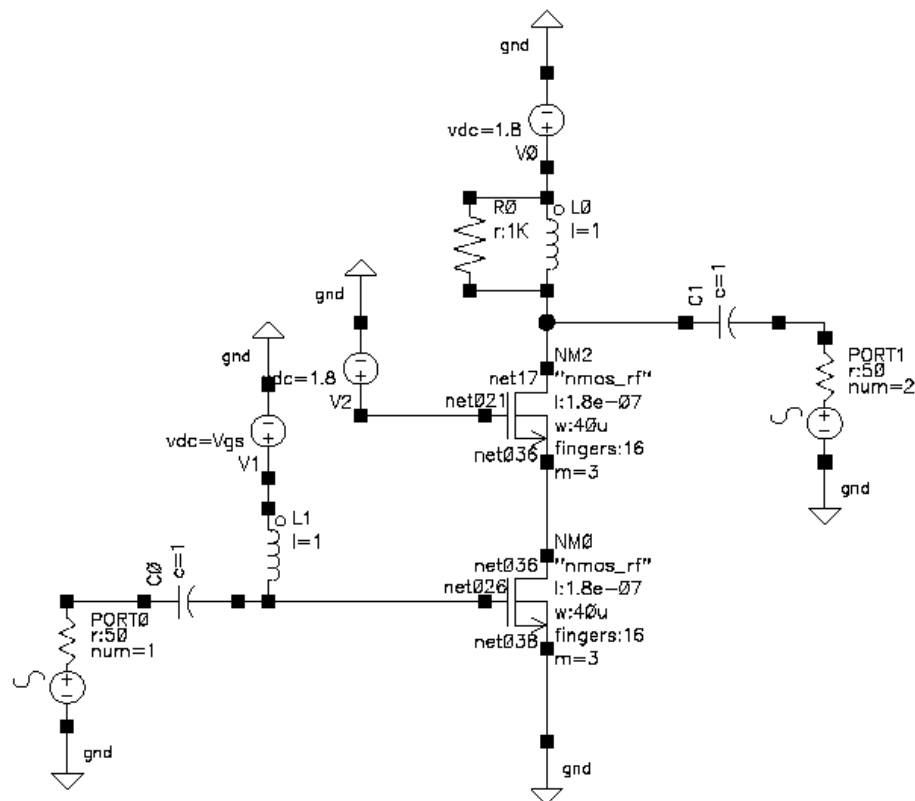a) Setup Environment

In the library named as LNA example, open new cell view named as Choose V_{GS} . Based on the knowledge conducted in the “Basis cadence lecture”, build the circuit as below.



- Highlight *input port* and modify it as

Edit Object Properties

OK Cancel Apply Defaults Previous Next Help

Apply To: ☐ only current ☐ instance

Show: ☐ system ☒ user ☒ CDF

Browse Reset Instance Labels Display

Property	Value	Display
Library Name	analogLib	off <input type="checkbox"/>
Cell Name	psin	off <input type="checkbox"/>
View Name	symbol	off <input type="checkbox"/>
Instance Name	PORT0	off <input type="checkbox"/>

Add Delete Modify

User Property	Master Value	Local Value	Display
IvsIgnore	TRUE		off <input type="checkbox"/>

CDF Parameter	Value	Display
Frequency name	F1	off <input type="checkbox"/>
Second frequency name		off <input type="checkbox"/>
Noise file name		off <input type="checkbox"/>
Number of noise/freq pairs	0	off <input type="checkbox"/>
Resistance	50 Ohms	off <input type="checkbox"/>
Port number	1	off <input type="checkbox"/>
DC voltage		off <input type="checkbox"/>
Source type	sine	off <input type="checkbox"/>
Delay time		off <input type="checkbox"/>
Sine DC level		off <input type="checkbox"/>

Typing in here

- Highlight *Output port* and modify it as

Edit Object Properties

OK Cancel Apply Defaults Previous Next Help

Apply To ☐ only current ☐ instance

Show ☐ system ☒ user ☒ CDF

Property Value Display

Library Name analogLib off ☐

Cell Name psin off ☐

View Name symbol off ☐

Instance Name PORT1 off ☐

User Property Master Value Local Value Display

Ivsignore TRUE off ☐

CDF Parameter Value Display

Frequency name F2 off ☐

Second frequency name off ☐

Noise file name off ☐

Number of noise/freq pairs 0 off ☐

Resistance 50 Ohms off ☐

Port number 2 off ☐

DC voltage off ☐


Source type sine off ☐

Delay time off ☐


Sine DC level off ☐

Typing in here

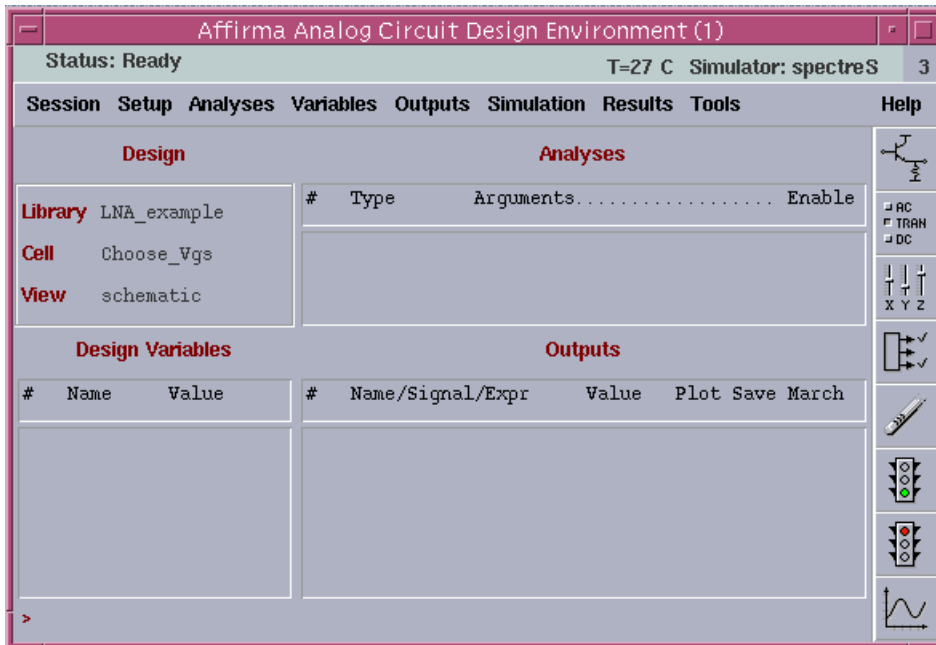- From the schematic window select: *Tool– Analog Environment*



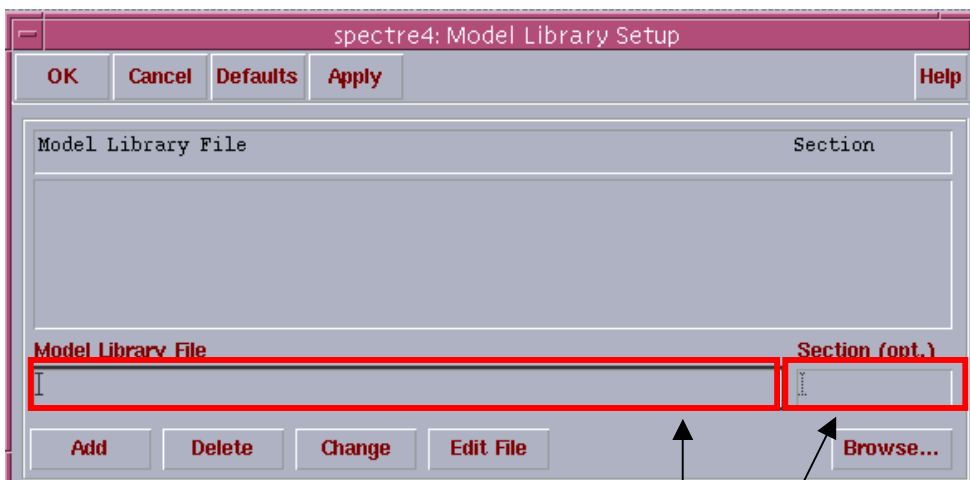- On the Analog Circuit Design Environment, Click *Setup–Model libraries*



Typing in here

- In the *Model Library File* and *Section* fields typing as following


Model Library File	Section (opt.)
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_3v
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_na
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_3vna
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_m
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_3m
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	ees
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_bip
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_bip3
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	dio
/data1/RACS/DC_project/Tsmc18/models/rf018.scs	tt_rfmos
/data1/RACS/DC_project/Tsmc18/models/ResModel.scs	res_t

➤ You can Click ***Browse*** and go up to the directory, which contain the model library of the technology you would like to use. Or instructors will introduce the path of model library

- **Notice:** After you finish typing one section, press ***Add*** icon. If you make some mistakes, you can delete by click ***Delete*** icon

- On the Analog Environment Window, Click *Variable–Copy from cell view*.

➤ Analog Environment window looks like

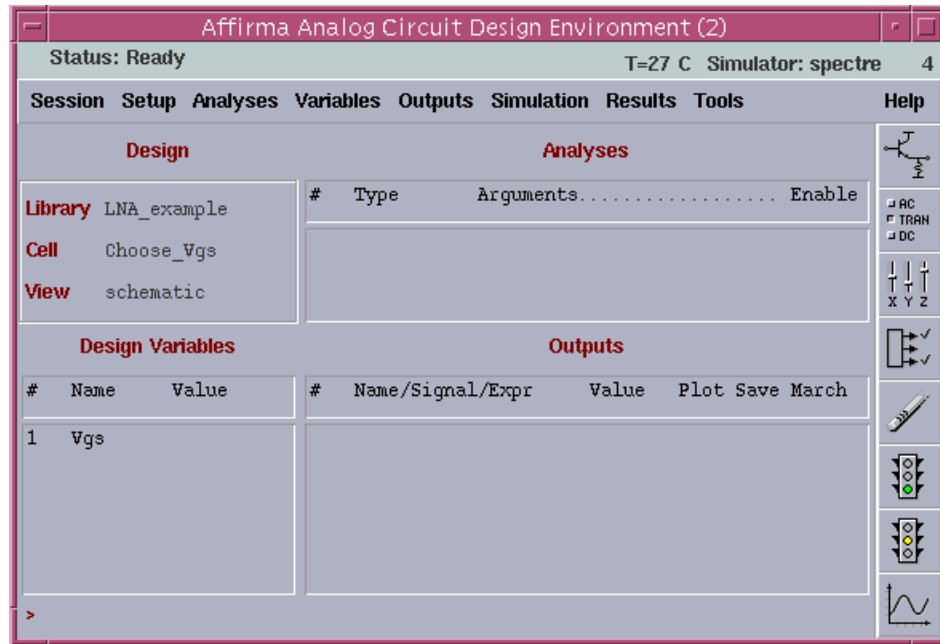


- Click edit variable icon on the right hand side




The following window will appear.

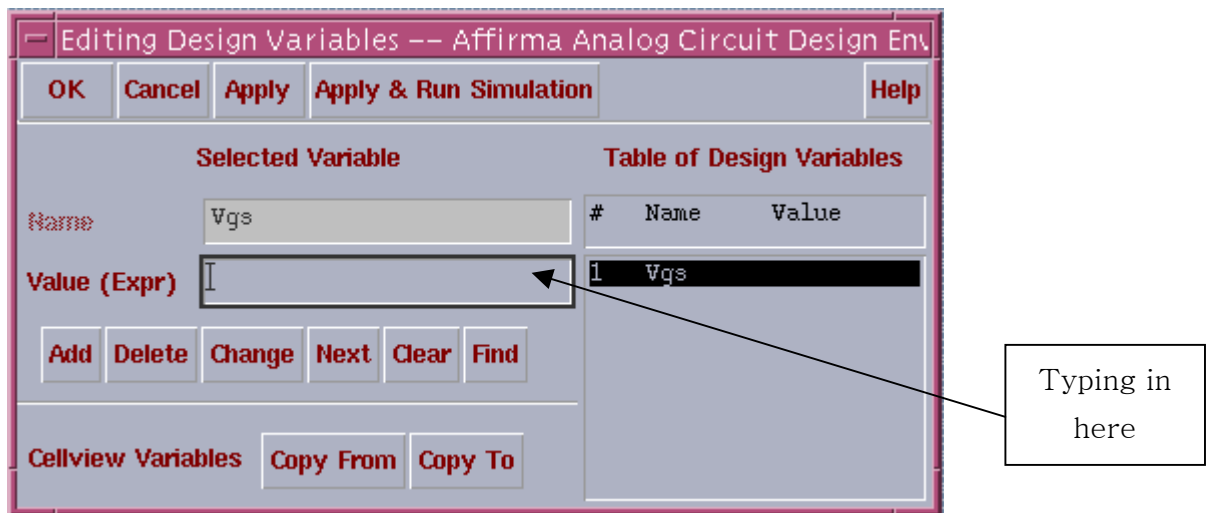- Highlight V_{GS} and typing its primary value (any value)




- On the Analog Circuit Design Environment, select *Analyses – Choose*.


The window will appear as

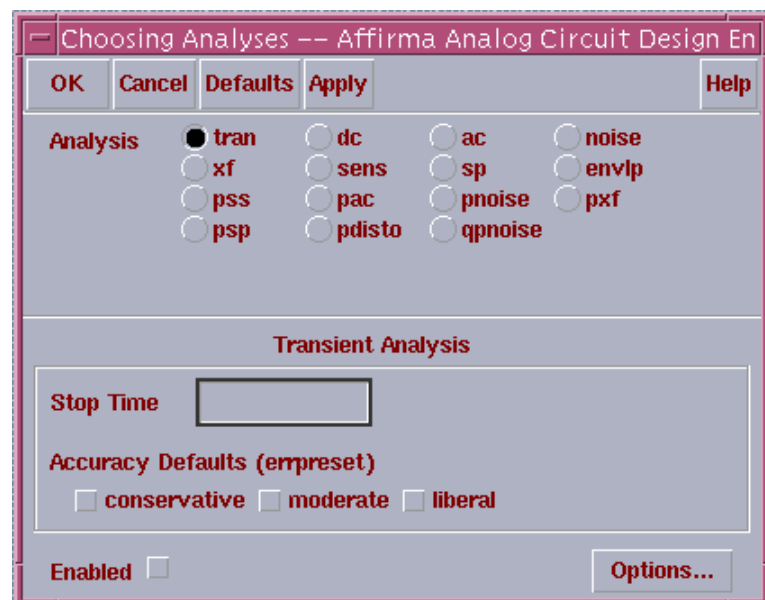

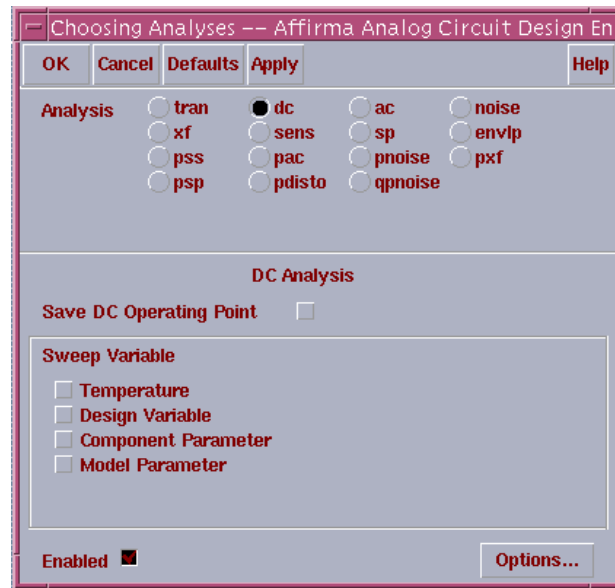
- On the choosing Analyses window, highlight *DC* simulator and modify the field as



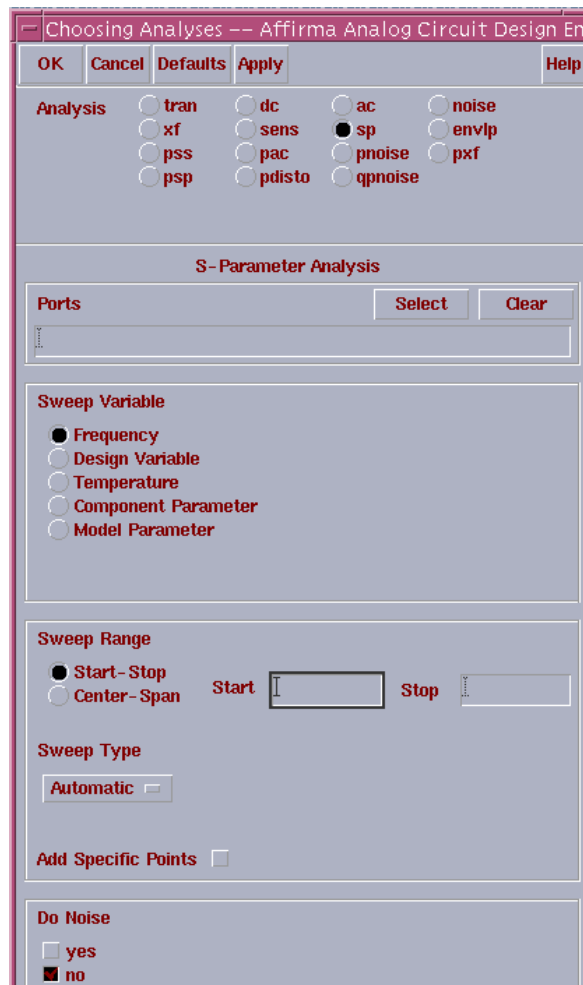- Click *Apply* icon.
- Choose *SP* Simulator, the window appear as



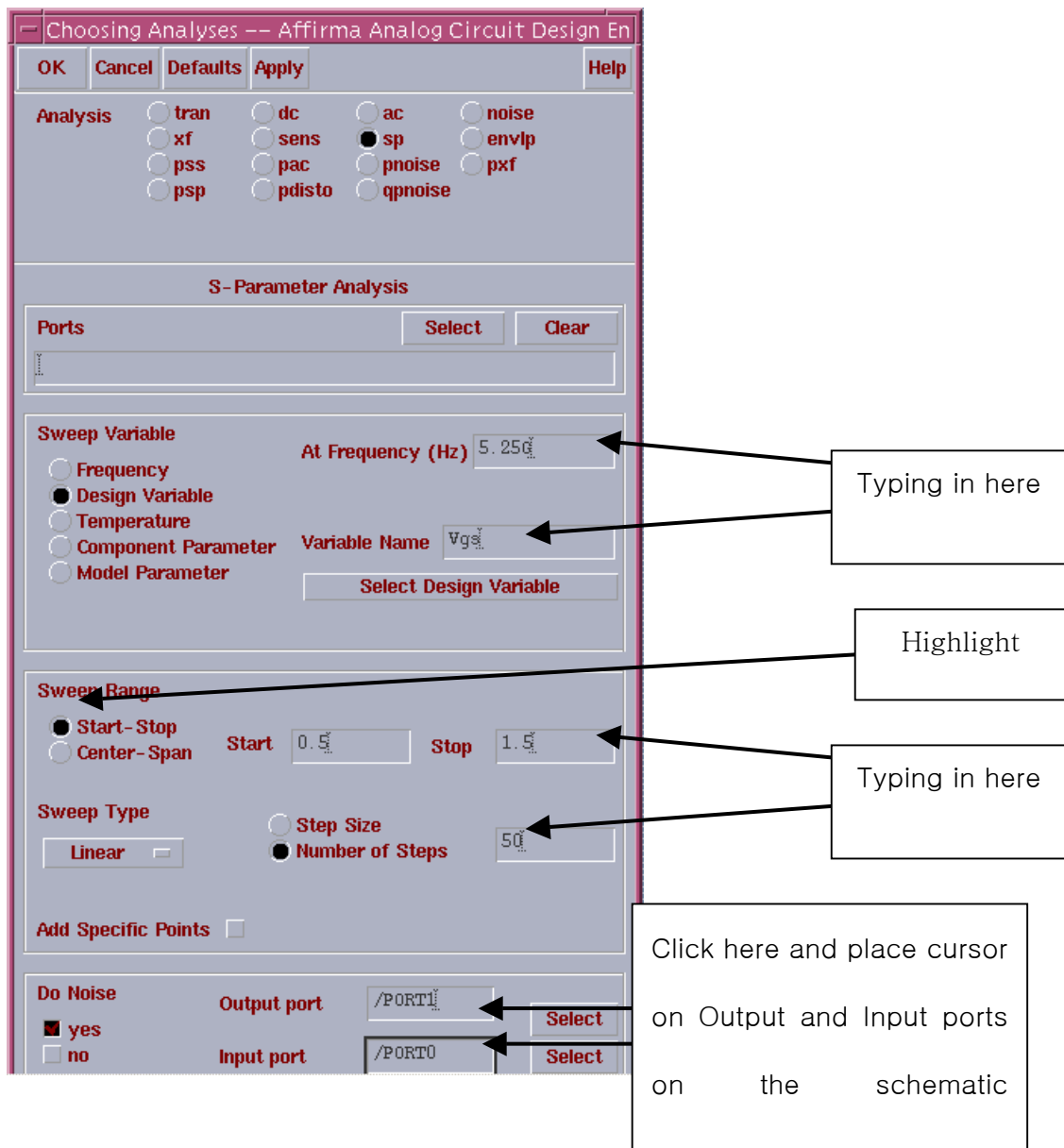- Modify your window to become as follows



- Click *OK*

b) Run simulation



- Click *Netlist and Run* icon
- After simulation is finished you can see the window looks like

```
File Help 5
/user/NTkien/simulation/Choose_Vgs/spectre/schematic/psf/spi

DC Analysis 'dcOp'
*****
Important parameter values:
reftol = 1e-03
abstol(I) = 1 pA
abstol(V) = 1 uV
temp = 25 C
tnom = 25 C
tempeffects = all
gmin = 1 pS
Convergence achieved in 2 iterations.
Total time required for dc analysis 'dcOp' was 0 s.


dcOpInfo: writing operating point information to rawfile.

*****
S-Parameter Analysis 'sp': freq = 5.25 GHz, Vgs = (500e-03 -> 2)
*****
sp: Vgs = 560e-03 (4 %), step = 30e-03 (2 %)
sp: Vgs = 620e-03 (8 %), step = 30e-03 (2 %)
sp: Vgs = 710e-03 (14 %), step = 30e-03 (2 %)
sp: Vgs = 770e-03 (18 %), step = 30e-03 (2 %)
sp: Vgs = 860e-03 (24 %), step = 30e-03 (2 %)
sp: Vgs = 920e-03 (28 %), step = 30e-03 (2 %)
sp: Vgs = 1.01 (34 %), step = 30e-03 (2 %)
sp: Vgs = 1.07 (38 %), step = 30e-03 (2 %)
sp: Vgs = 1.16 (44 %), step = 30e-03 (2 %)
sp: Vgs = 1.22 (48 %), step = 30e-03 (2 %)
sp: Vgs = 1.31 (54 %), step = 30e-03 (2 %)
sp: Vgs = 1.37 (58 %), step = 30e-03 (2 %)
sp: Vgs = 1.46 (64 %), step = 30e-03 (2 %)
sp: Vgs = 1.52 (68 %), step = 30e-03 (2 %)
sp: Vgs = 1.61 (74 %), step = 30e-03 (2 %)
sp: Vgs = 1.67 (78 %), step = 30e-03 (2 %)
sp: Vgs = 1.76 (84 %), step = 30e-03 (2 %)
sp: Vgs = 1.82 (88 %), step = 30e-03 (2 %)
sp: Vgs = 1.91 (94 %), step = 30e-03 (2 %)
sp: Vgs = 1.97 (98 %), step = 30e-03 (2 %)
Accumulated DC solution time = 20 ms.
Intrinsic sp analysis time = 590 ms.
Total time required for sp analysis 'sp' was 610 ms.

modelParameter: writing model parameter values to rawfile.
element: writing instance parameter values to rawfile.
```

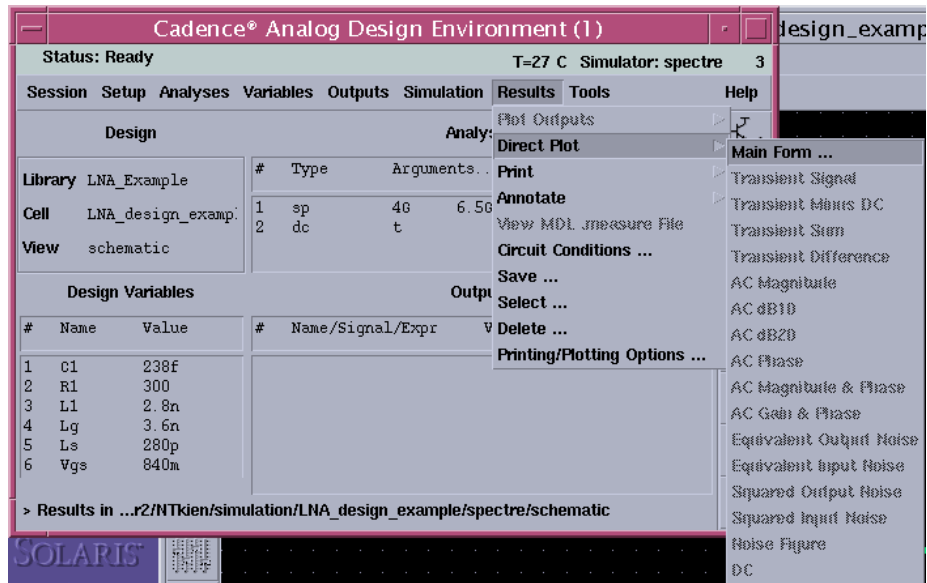c) Plotting Results

- In the Simulation window, select *Results* → *Direct Plot* → *Main Form*.




- The window will appear as



- On the *SP-Parameters Result Form*, do following

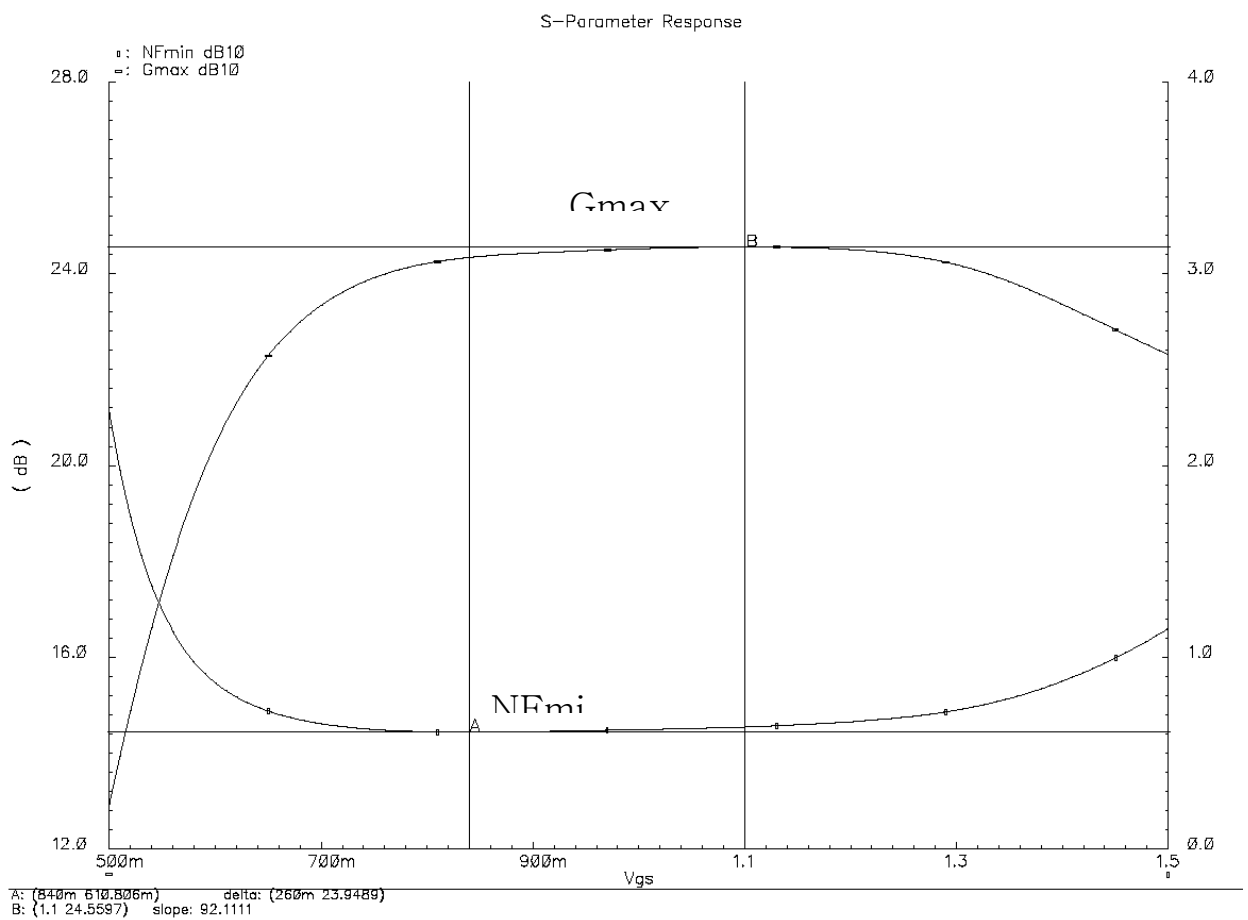- Highlight *Append* for *Plot Mode*
- Highlight *Gmax* for *Function*
- Highlight *Rectangular* for *Plot Type*
- Highlight *dB10* for *Modifier*
- Click *Plot*
- Choose *NFmin* for *Function*
- Highlight *Rectangular* for *Plot Type*
- Highlight *dB10* for *Modifier*
- Click *Plot*



From above figures, we can determine the value of V_{gs} that gives the minimum

NF and maximum available gain. As can be seen in this figure, we choose $V_{gs} = 840$ mV.

2) Choose Size of Transistor


❖ Choose the size of transistor by simulating $\Gamma_{opt} = 50 \Omega$ factor

a) Setup environment

We can set the multiplier factor of transistor as a variable and do the simulation to find the optimum value. But in this process the multiplier cannot be a variable therefore we have to do some simulation steps to find the optimum value of multiplier factor.

➤ Setting the simulation window as

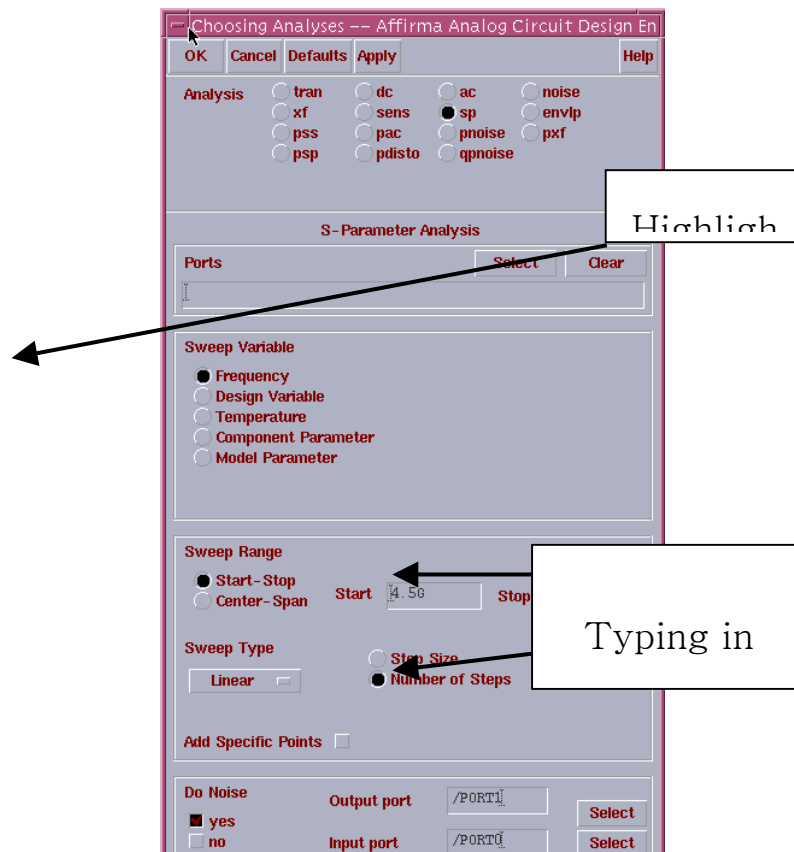
- Setting $V_{gs} = 840$ mV.
- Modify SP simulator as below.



- Click *OK*

b) Run Simulation

- Click *Run* simulation icon

 

c) Plotting Results

- After simulation finish click *Results* → *Main For* → *S-parameters*.
- On the *S-Parameter* Results window do following
 - Choose *Gmin* (Optimum noise Reflection Coefficient) for *Function*
 - Choose *Z-Smith* for *Plot Type*

S-Parameter Results

OK Cancel Help

Plot Mode ☒ Append ☐ Replace

Function

<input type="radio"/> SP	<input type="radio"/> ZP	<input type="radio"/> YP	<input type="radio"/> HP
<input type="radio"/> GD	<input type="radio"/> VSWR	<input type="radio"/> NFmin	<input checked="" type="radio"/> Gmin
<input type="radio"/> Rn	<input type="radio"/> m	<input type="radio"/> NF	<input type="radio"/> Kf
<input type="radio"/> B1f	<input type="radio"/> GT	<input type="radio"/> GA	<input type="radio"/> GP
<input type="radio"/> Gmax	<input type="radio"/> Gmsg	<input type="radio"/> Gumx	
<input type="radio"/> ZM	<input type="radio"/> NC	<input type="radio"/> GAC	
<input type="radio"/> GPC	<input type="radio"/> LSB	<input type="radio"/> SSB	

Description: Optimum Noise Reflection Coefficient

Plot Type ☐ Auto ☐ Rectangular

☒ Z-Smith ☐ Y-Smith

☐ Polar


Plot

Add To Outputs ☐

> Press "Plot" button to plot...

- Click *Plot*

□: Gmin

 


Another way to see the result

- On the Analog Circuit Design Environment, do following
 - Highlight *ZP* (Z parameters) for *Function*
 - Highlight *Rectangular* for *Plot Type*
 - Highlight *Real* for *Modifier*



 - Click *Z11* we can see the results as below



➤ On the Schematic window do following


- Highlight *NMOS* transistor by press *Q*
- On the properties window, change *multiplier* = 2.

Typing in


- Press *OK*

- Press *Save and Check* icon

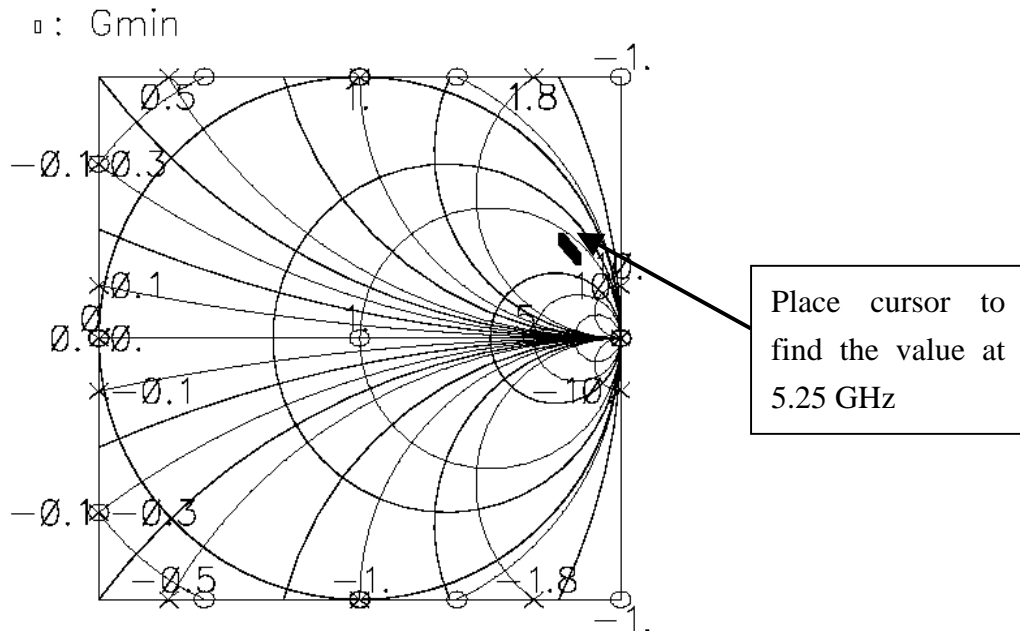Run simulation and plot result (do the same steps as previous)





- Do the same step to plot the Z_{11}

 

- Do the same above steps for *multiplier* = 3, you obtain the result as



□: Gmin

  

A: (5.25G 42.1331)

- Do the same above steps for *multiplier* = 4, you obtain the result as

□: G_{min}

  

A: (5.25G 31.5987)


As can be seen from above figures, when **multiplier** factor = 3, the real part of $G_{min} = 1$.

3) Choose L_s (Inductor Degeneration)

This step is to choose the value of L_s that makes the real part of $S_{11} = 1$

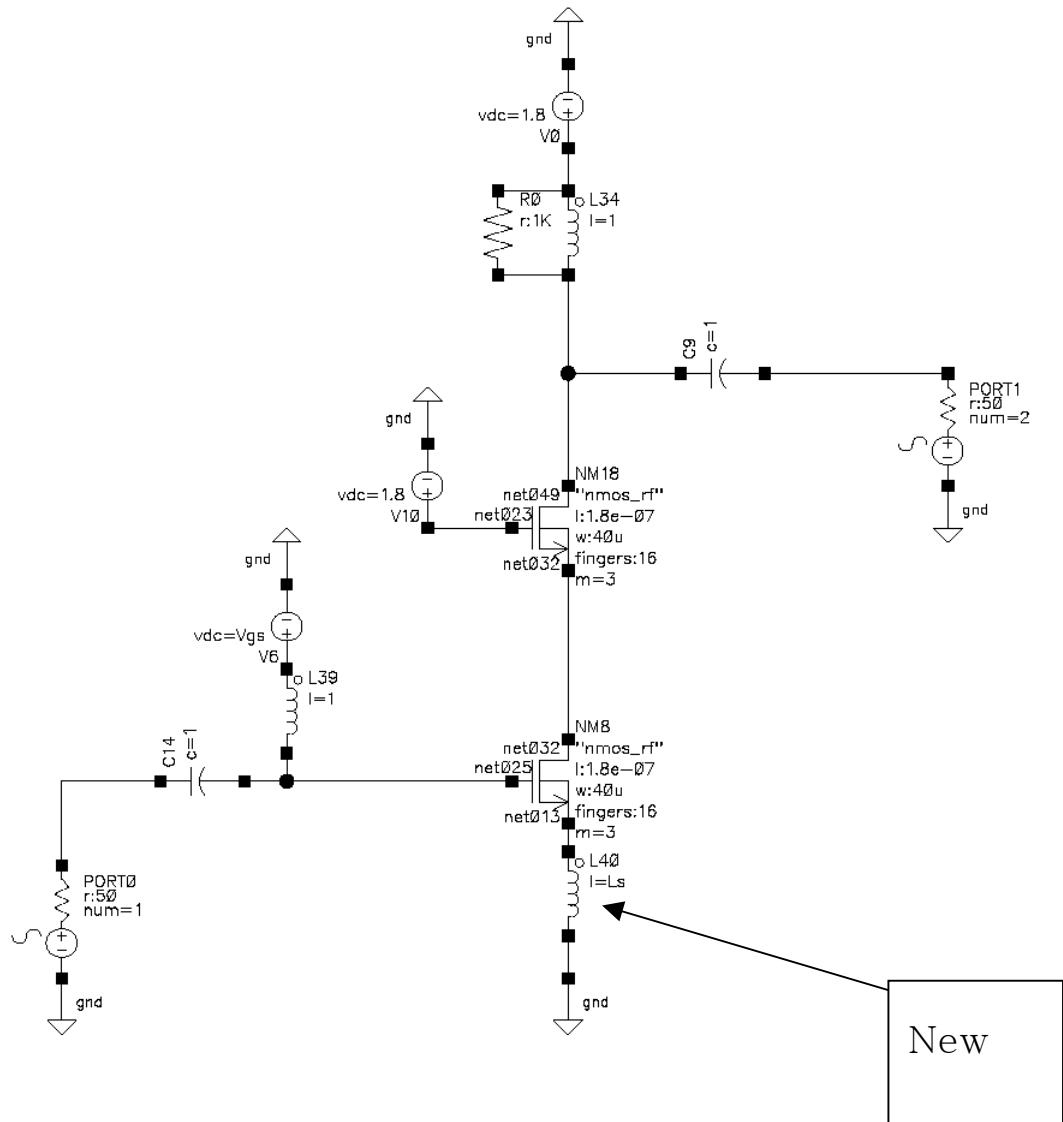
a) Setup Environment

- In the schematic window, insert new inductor as below




- A new inductor has inductance value as L_s
- On the Analog Circuit Design Environment do the following
 - Select Variables – Copy From Cell View
 - Setting primary value of L_s (any value)

- Modify *SP* simulation looks like

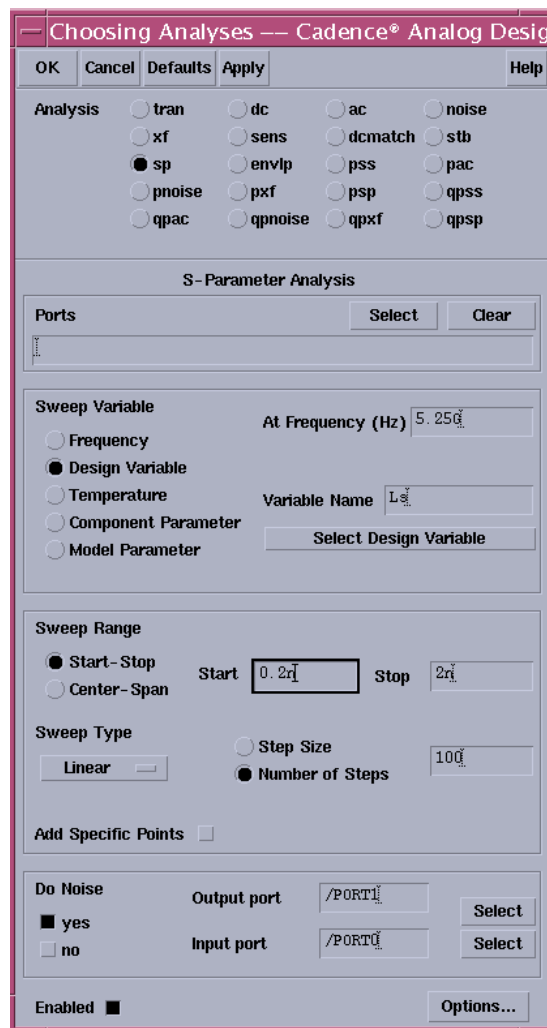

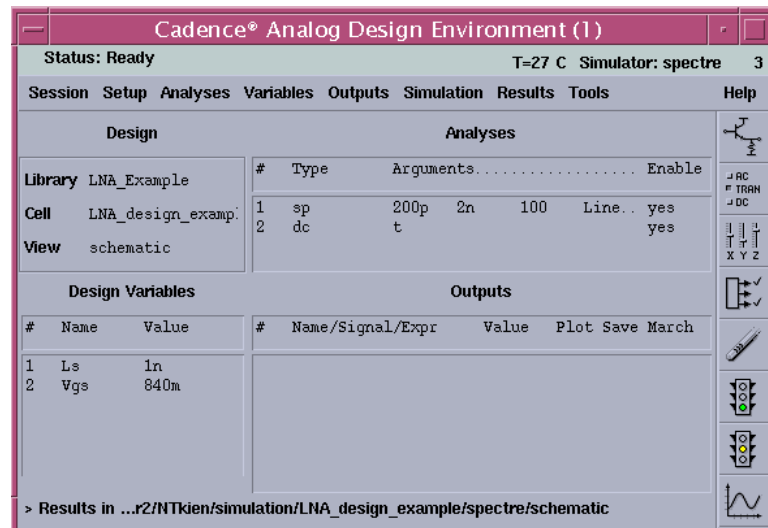- Click *OK*
- Now your Circuit Design Environment looks like



b) Run Simulation

- Click *Netlist and Run* icon




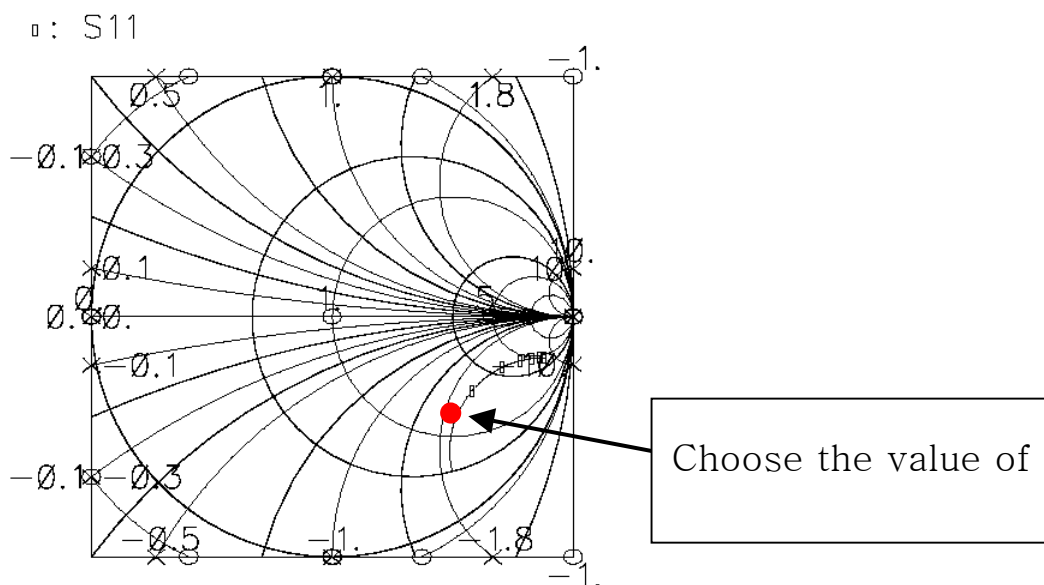c) Plotting Results

- After finish simulation, select *Results* → *Direct Plot* → *Main Form*
- On the *S-Parameter Results* window do following
 - Highlight *SP* (S parameters) for *Function*
 - Highlight *Z-Smith* for *Plot Type*



➤ Click ***S11***, you can see the result as below




From this figure, you obtain the value of $L_s = 0.28 \text{ nH}$

4) Choose the series gate inductance

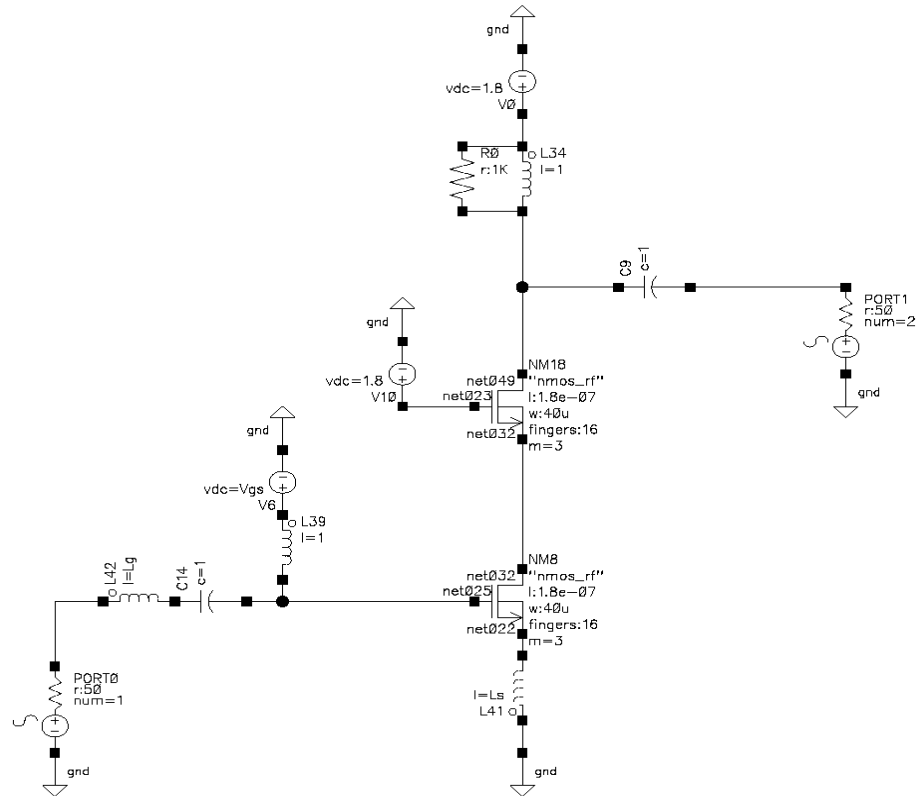a) Setup environment

- Insert new inductor which has the inductance value = L_g .



- On the *Analog Circuit Design Environment*, do the following
 - Change the value of $L_s = 0.28$ nH.
 - Select *Variable – Copy From Cell View*.
 - Set the primary value of L_g (any value)
 - In the Analog Circuit Design Environment, double click on the SP simulation and modify as

Choosing Analyses --- Cadence® Analog Design

OK Cancel Defaults Apply Help

Analysis

☐ tran ☐ dc ☐ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ stb
☒ sp ☐ envlp ☐ pss ☐ pac
☐ pnoise ☐ pxf ☐ psp ☐ qpss
☐ qpac ☐ qpnoise ☐ qpxf ☐ qpssp

S-Parameter Analysis

Ports

Sweep Variable

☐ Frequency ☐ Design Variable ☐ Temperature ☐ Component Parameter ☐ Model Parameter

At Frequency (Hz)

Variable Name

Sweep Range

☒ Start-Stop ☐ Center-Span

Start Stop

Sweep Type

☐ Step Size ☒ Number of Steps

Linear

Add Specific Points ☐

Do Noise


☒ yes ☐ no

Output port

Input port

Enabled ☒

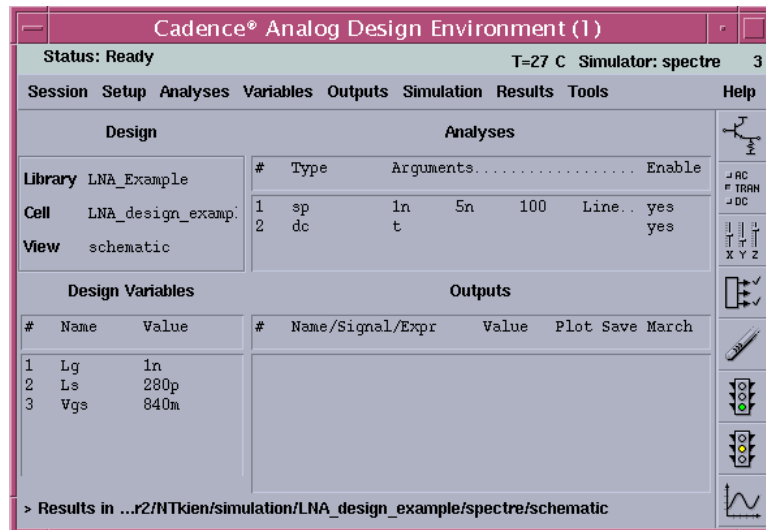- Click *OK*
- Now the Analog Circuit Design Environment becomes as below



b) Run Simulation

- Click *Netlist and Run* icon



c) Plotting Results

- After finish simulation, select *Results* → *Direct Plot* → *Main Form* → *S-parameters*.
- On the *S-Parameter Results* window do following
 - Highlight *SP* (S parameters) for *Function*
 - Highlight *Z-Smith* for *Plot Type*

S-Parameter Results

OK Cancel Help

Plot Mode ☒ Append ☐ Replace

Function

☒ SP ☐ ZP ☐ YP ☐ HP
☐ GD ☐ VSWR ☐ NFmin ☐ Gmin
☐ Rn ☐ m ☐ NF ☐ Kf
☐ B1f ☐ GT ☐ GA ☐ GP
☐ Gmax ☐ Gmsg ☐ Gumx
☐ ZM ☐ NC ☐ GAC
☐ GPC ☐ LSB ☐ SSB

Description: S-Parameter


Plot Type ☐ Auto ☐ Rectangular
☒ Z-Smith ☐ Y-Smith
☐ Polar

S11 S12
S21 S22

Add To Outputs ☐

> Press Sij-button to plot...

 
- Click **S11**, you can see the result as below



5) Output Matching: Choose load inductance and load resistance

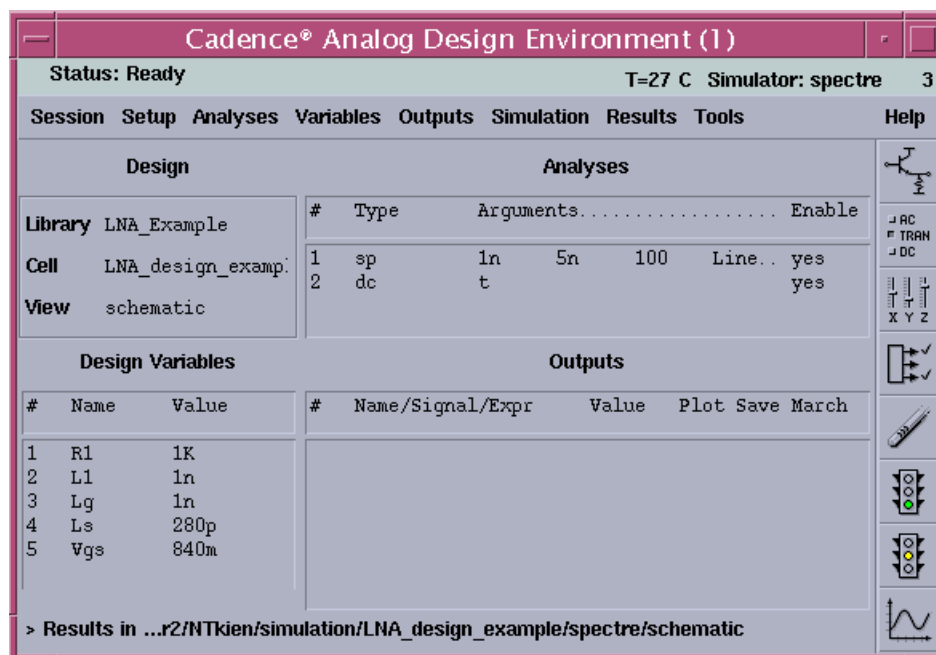a) Setup environment

- On the Schematic Window do following steps
 - Change the value of the load resistor to become R1
 - Chang the value of the load inductor to become L1
- On the *Analog Circuit Design Environment* do following
 - Click *Variables → Copy From Cell View*
 - Set the *primary value* of L1 and R1 (any value)
 - The Analog Design Environment look like



- Double Click on the SP simulator and modify it as

Choosing Analyses --- Cadence® Analog Design

OK Cancel Defaults Apply Help

Analysis ☐ tran ☐ dc ☐ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ stb
☒ sp ☐ envlp ☐ pss ☐ pac
☐ pnoise ☐ pxf ☐ psp ☐ qpss
☐ qpac ☐ qpnoise ☐ qpxf ☐ qpssp

S-Parameter Analysis

Ports

Sweep Variable ☐ Frequency ☒ Design Variable ☐ Temperature ☐ Component Parameter ☐ Model Parameter
At Frequency (Hz) 5.25GHz
Variable Name L1

Sweep Range ☒ Start-Stop ☐ Center-Span
Start 1GHz Stop 5GHz
Sweep Type ☐ Step Size ☒ Number of Steps
Linear 100

Add Specific Points ☐

Do Noise ☒ yes ☐ no
Output port /PORT1
Input port /PORT2

Enabled ☒

➤ Select *Tools – Parametric Analysis*, the following window appears

Parametric Analysis – spectre(1): LNA_example Cascode schematic


Tool Setup Analysis Help 43

Sweep 1 Variable Name

Range Type From To Select ☐

Step Control Total Steps

- Modify the window as below

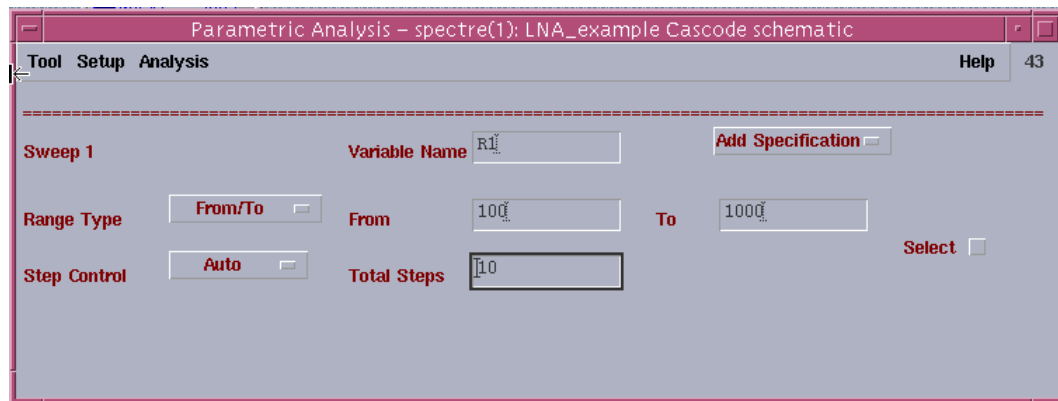

b) Run Simulation

- On the Parametric Analysis window, select *Analysis – Start*

c) Plotting Results

- After simulation is finished, Plotting result
- On the Analog Circuit Design Environment, choose: *Results → Direct Plot → Main Form → S-parameters*, the *SP-Parameters* window will appear
- Highlight *SP* for *Function*
- Highlight *Z-Smith* for *Plot Type*
- Click *S22* button

➤ Based on above figure, assume that you decide to design LNA has gain around 18, so result shows the value of $R1 = 300 \text{ Ohm}$.

➤ See in the Smith chart, when the $R1 = 300 \text{ Ohm} \rightarrow L1 = 2.8 \text{ nH}$

6) Output Matching: choose output capacitance

a) Setup environment

➤ On the schematic window, *highlight* capacitor named $C1$ and setting its *capacitance* value = $C1$.

➤ On the Analog Circuit Design Environment, do following

- Select *Variable – Copy From Cell View*.
- Set the primary value of $C1$ (any value)
- Change the value of $L1 = 2.8 \text{ nH}$ (this result is obtained in the previous simulation step)
- On the *Analog Circuit Design Environment* window, double click on the SP simulation and modify as

Choosing Analyses — Cadence® Analog Design

OK Cancel Defaults Apply Help

Analysis

☐ tran ☐ dc ☐ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ stb
☒ sp ☐ envlp ☐ pss ☐ pac
☐ pnoise ☐ pxf ☐ psp ☐ qpss
☐ qpac ☐ qpnoise ☐ qpxf ☐ qpssp

S-Parameter Analysis

Ports Select Clear

Sweep Variable At Frequency (Hz) 5.25GHz

☐ Frequency
☒ Design Variable
☐ Temperature
☐ Component Parameter
☐ Model Parameter

Variable Name c1 Select Design Variable

Sweep Range

☒ Start-Stop Start 100f Stop 500f
☐ Center-Span

Sweep Type

☐ Step Size 100
☒ Number of Steps

Add Specific Points ☐

Do Noise

☒ yes ☐ no
 Output port /PORT1 Select
 Input port /PORT1 Select

Enabled ☒ Options...

➤ Now your Analog Circuit Design Environment looks like below

Cadence® Analog Design Environment (1)

Status: Ready T=27 C Simulator: spectre 3

Session Setup Analyses Variables Outputs Simulation Results Tools Help

Design			Analyses			
Library	Cell	View	#	Type	Arguments.....	Enable
LNA_Example	LNA_design_examp	schematic	1	sp	100f 500f 100	Line.. yes
			2	dc	t	yes

Design Variables			Outputs			
#	Name	Value	#	Name/Signal/Expr	Value	Plot Save March
1	c1	1				
2	R1	300				
3	L1	2.8n				
4	Lg	3.6n				
5	Ls	280p				
6	Vgs	840m				

> Results in ...r2/NTkien/simulation/LNA_design_example/spectre/schematic

b) Run simulation

- Click *Netlist and Run* icon




c) Plotting result


- After finish simulation, select *Results* → *Direct Plot* → *Main Form* → S

Parameters

- On the *S-Parameter Results* window do following
 - Highlight *SP* for *Function*
 - Highlight *Z-Smith* for *Plot Type*

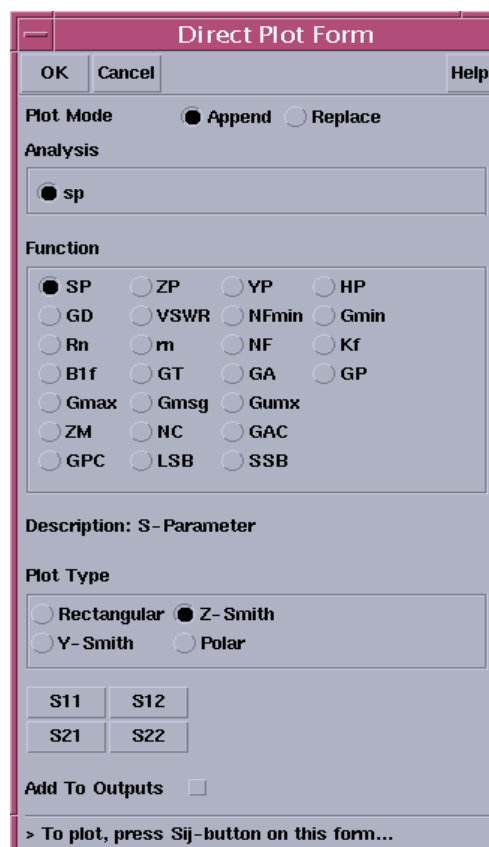A screenshot of the "Direct Plot Form" dialog box. It has a title bar with a minus sign, a maximize button, and a close button. Below the title bar are "OK", "Cancel", and "Help" buttons. The "Plot Mode" section has two radio buttons: "Append" (selected) and "Replace". The "Analysis" section has a dropdown menu with "sp" selected. The "Function" section has a grid of radio buttons: SP (selected), ZP, YP, HP, GD, VSWR, NFmin, Gmin, Rn, rm, NF, Kf, B1f, GT, GA, GP, Gmax, Gmsg, Gumx, ZM, NC, GAC, GPC, LSB, and SSB. The "Description: S-Parameter" section is below. The "Plot Type" section has three radio buttons: Rectangular, Z-Smith (selected), Y-Smith, and Polar. Below this are four buttons: S11, S12, S21, and S22. At the bottom, there is a checkbox for "Add To Outputs" and a text field containing "> To plot, press Sij-button on this form...".

 
- Click **S22** button, you can see the result as below



7) Running S-Parameters and NF Simulation

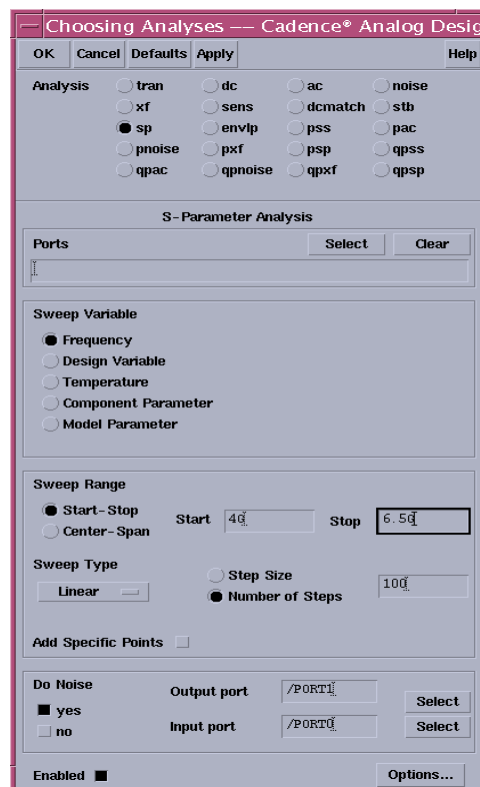
a) Setup Environment

- On the Analog Circuit Design Environment window, do following
 - Change the value of C1 = 238 fF
 - Double click on SP simulator and modify it as



Click **OK**

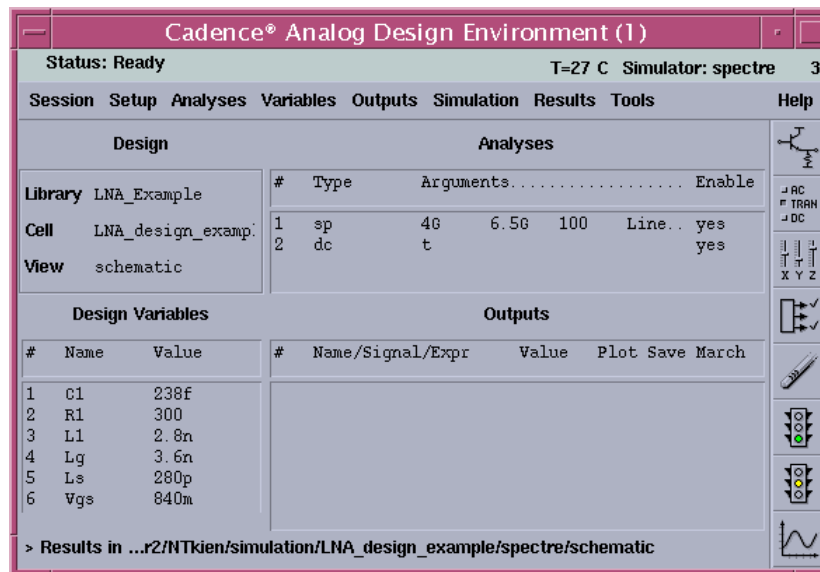- Now the Analog Circuit Design Environment looks like below



- b) Run simulation

Click The *Netlist and Run* icon to run the simulation



- c) Plotting Results

❖ *Plot S parameters:*

On the Analog Design Environment window

- Click *Results → Direct Plot → Main Form → S Parameters*
- Modify *Direct Plot Form* window as follows

Direct Plot Form

OK Cancel Help

Plot Mode ☒ Append ☐ Replace

Analysis
☒ sp

Function
☒ SP ☐ ZP ☐ YP ☐ HP
☐ GD ☐ VSWR ☐ NFmin ☐ Gmin
☐ Rn ☐ m ☐ NF ☐ Kf
☐ B1f ☐ GT ☐ GA ☐ GP
☐ Gmax ☐ Gmsg ☐ Gumx
☐ ZM ☐ NC ☐ GAC
☐ GPC ☐ LSB ☐ SSB

Description: S-Parameter

Plot Type
☒ Rectangular ☐ Z-Smith
☐ Y-Smith ☐ Polar


Modifier
☐ Magnitude ☐ Phase ☒ dB20
☐ Real ☐ Imaginary

S11 S12
S21 S22

Add To Outputs ☐

> To plot, press Sij-button on this form...

 - Click on S11, S22, S21, and S12 separately, the results are shown as follows



As can be seen in above Fig., the value of S_{11} is high because the limitation of the isolation between output and input. However, the value of $S_{11} = 15$ dB, it can be accepted. If the value of S_{11} is higher than -15 dB, the designer might have to do some simulation steps.

- Keep the output matching as the condition which is found at step (5) & (6)
- Find the value of L_s as the step (3).
- Find the value of L_g as the step (4)

❖ *Plot NF and NFmin of LNA*

On the Direct Plot Form

- Highline *NFmin* (or *NF*) at the function field
- Highline *dB10* for Modified

Direct Plot Form

OK Cancel Help

Plot Mode ☒ Append ☐ Replace

Analysis

☒ sp

Function

☐ SP ☐ ZP ☐ YP ☐ HP
☐ GD ☐ VSWR ☒ NFmin ☐ Gmin
☐ Rn ☐ m ☐ NF ☐ Kf
☐ B1f ☐ GT ☐ GA ☐ GP
☐ Gmax ☐ Gmsg ☐ Gumx
☐ ZM ☐ NC ☐ GAC
☐ GPC ☐ LSB ☐ SSB

Description: Minimum Noise Factor

Modifier

☐ Magnitude ☒ dB10

Add To Outputs ☐ Plot

> Press plot button on this form...

Direct Plot Form

OK Cancel Help

Plot Mode ☒ Append ☐ Replace

Analysis

☒ sp

Function

☐ SP ☐ ZP ☐ YP ☐ HP
☐ GD ☐ VSWR ☐ NFmin ☐ Gmin
☐ Rn ☐ m ☒ NF ☐ Kf
☐ B1f ☐ GT ☐ GA ☐ GP
☐ Gmax ☐ Gmsg ☐ Gumx
☐ ZM ☐ NC ☐ GAC
☐ GPC ☐ LSB ☐ SSB

Description: Noise Figure


Modifier

☐ Magnitude ☒ dB10

Add To Outputs ☐ Plot

> Press plot button on this form...

The results are shown as follows

 

As can be in above Figures, the value of the NF is slightly higher than NF_{\min} of the given topology. The reason is the size of the input transistor cannot be chosen properly.

(See the choosing transistor size step, *step (2)*)

8) Linearity simulation (IIP3 and 1 dB compression Point)

a) Setup environment

- On the schematic window, highlight *input Port* and *modify* it as


Property	Value	Display
Library Name	analogLib1	off
Cell Name	psir1	off
View Name	symbol1	off
Instance Name	PORT1	off

User Property	Master Value	Local Value	Display
IvsIgnore	TRUE		off


CDF Parameter	Value	Display
Frequency name	F1	off
Second frequency name		off
Noise file name		off
Number of noise/freq pairs	0	off
Resistance	50 Ohms	off
Port number	1	off
DC voltage		off
Source type	sine	off
Delay time		off
Sine DC level		off
Amplitude		off
Amplitude (dBm)	rf_pwr	off
Initial phase for Sinusoid		off
Frequency	rf_freq Hz	off
Amplitude 2		off

Amplitude 2 (dBm)		off
Initial phase for Sinusoid 2		off
Frequency 2		off
FM modulation index		off
FM modulation frequency		off
AM modulation index		off
AM modulation frequency		off
AM modulation phase		off
Damping factor		off
Multiplier		off
Temperature coefficient 1		off
Temperature coefficient 2		off
Nominal temperature		off
Noise temperature		off
AC magnitude		off
AC phase		off
XF magnitude		off
PAC magnitude		off
PAC magnitude (dBm)	rf_pwr	off

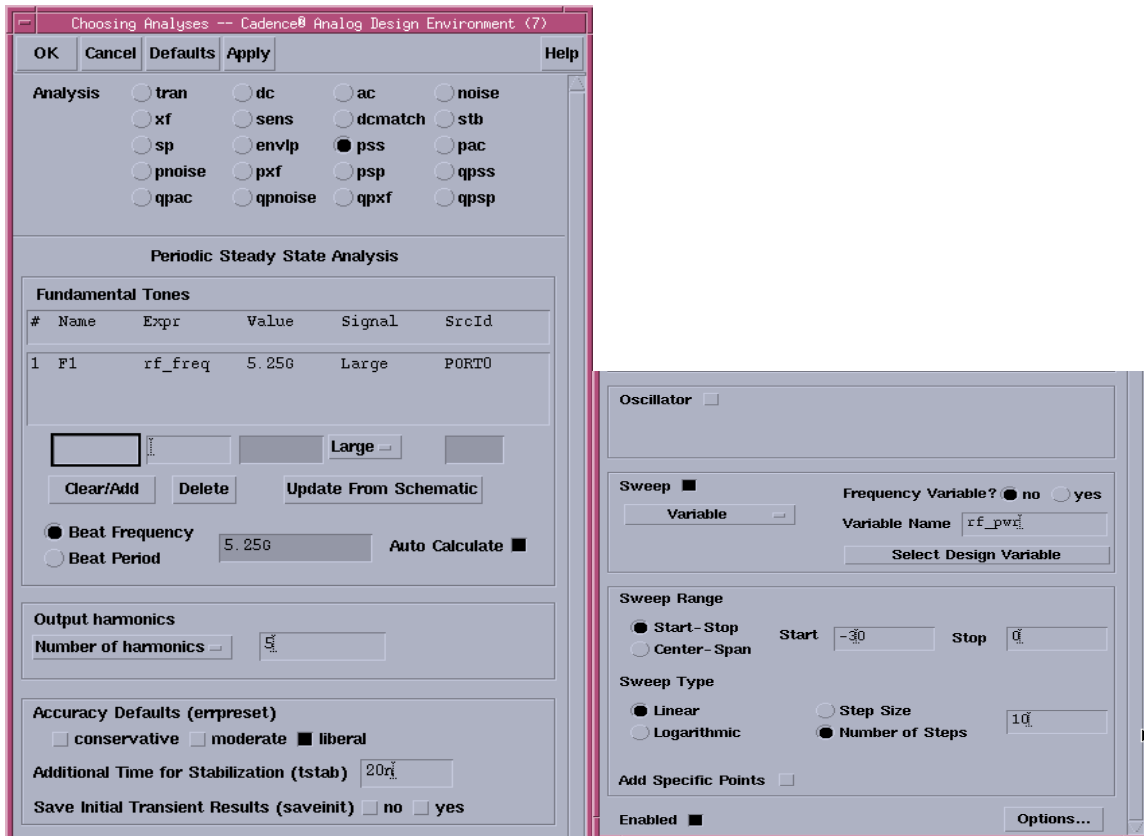- On the Analog Circuit Design Environment do following
- *Select Variable – Copy From Cell View*
- Setting the primary value of *rf_freq* and *rf_pwr* to be *5.25 G* and *-40*
- Select *Analyses – Choose*
- Highlight *PSS* and *modify* it as below




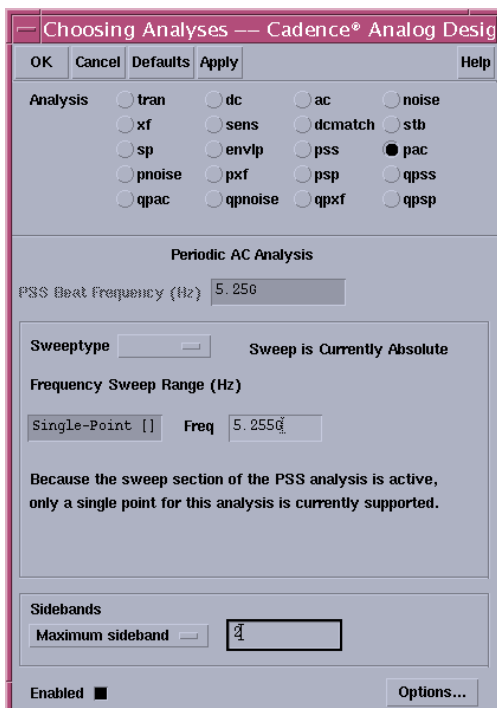- Highlight *PAC* on the *Choosing Analyses* window and modify it as



- Click *OK* on the *Choosing Analyses* window.

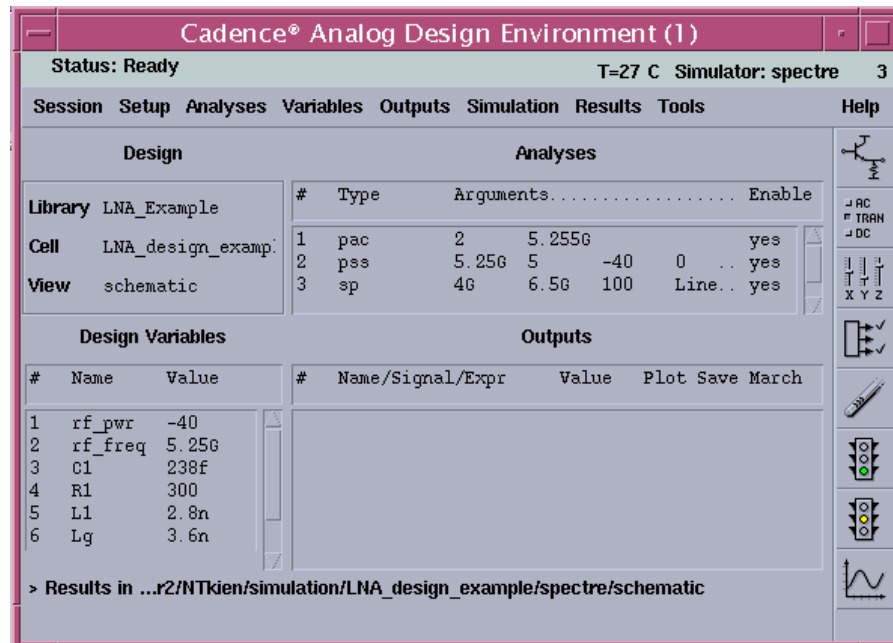- Your Analog Circuits Design Environment looks like



b) Run simulation

- To run SP analysis, click *Netlist and Run* icon



- Look in the output log file to be sure the simulation is completed successfully.

c) Plotting Results

❖ Plotting 1 dB compression point

- In the simulation window, choose *Results* → *main Plot* → *PSS*. The Waveform window and PSS results form appear.
- In the PSS results, highlight *PSS* for *Analysis Type*
- In the PSS results, highlight *Compression* point for *Function*

- Highlight *Variable Sweep* for circuit input power

Direct Plot Form

OK Cancel Help

Plot Mode ☒ Append ☐ Replace

Analysis

☐ sp ☒ pss ☐ pac

Function

☐ Voltage ☐ Current

☐ Power ☐ Voltage Gain

☐ Current Gain ☐ Power Gain

☐ Transconductance ☐ Transimpedance

☒ Compression Point ☐ IPN Curves

☐ Power Contours ☐ Reflection Contours

☐ Harmonic Frequency ☐ Power Added Eff.

☐ Power Gain Vs Pout ☐ Comp. Vs Pout

☐ Node Complex Imp.

Select Port (fixed R(port))

Format Output Power

Gain Compression (dB) 1

"rf_pwr" ranges from -30 to 0

Input Power Extrapolation Point (dBm) -30

Input Referred 1dB Compression


1st Order Harmonic

0	0
1	5.25G
2	10.5G
3	15.75G
4	21G
5	26.25G

Add To Outputs ☐

> Select Port on schematic...

 - Place cursor in the schematic window and click on the **output port**.



❖ *Plotting IIP3*

- On the *Analog Circuit Design Environment* window, choose: **Results** → **Direct Plot** → **PSS**. The waveform window and the PSS results appear
- Highlight **PAC** and modify it as

Direct Plot Form

OK Cancel Help

Plot Mode ☒ Append ☐ Replace

Analysis

☐ sp ☐ pss ☒ pac

Function

☐ Voltage ☐ Current

☒ IPN Curves

Select Port (fixed R(port))

Circuit Input Power ☐ Single Point

☒ Variable Sweep ("rf_pwr")

"rf_pwr" ranges from -30 to 0

Input Power Extrapolation Point (dBm) -30

Input Referred IP3 Order 3rd


3rd Order Harmonic		1st Order Harmonic	
-2	5.245G	-2	5.245G
-1	5M	-1	5M
0	5.255G	0	5.255G
1	10.505G	1	10.505G
2	15.755G	2	15.755G

Add To Outputs ☐ Replot


freqaxis = absout

> Select Port on schematic...

 - Place cursor on the output port in the schematic window, you will see the result as



 ➤ If we choose the Extrapolation value is -20, then we obtain the following Fig.



✓ SNIM technique is applicable for any Z_s with assuming

$$R_n = R_n^o = \frac{\gamma}{\alpha} \cdot \frac{1}{g_m}, \quad Z_{opt} = Z_{opt}^o - sL_s$$

$$F_{min} = F_{min}^o = 1 + \frac{2}{\sqrt{5}} \frac{\omega}{\omega_T} \sqrt{\gamma \delta (1 - |c|^2)}$$

Stays valid with large W , high P_D and ω

✓ Problem occurs with small W (low P_D) and low ω

→ increase $\text{Re}[Z_{opt}]$ → requires high $\text{Re}[Z_{in}^*] = \text{Re}[Z_{opt}]$

→ requires high L_s → makes the expression for F_{min} invalid

→ F_{min} increase significantly above F_{min}^o

✓ Even with small W , low P_D , and low ω , possible to achieve $Z_s = Z_{in}^*$ with L_s but $\text{NF} > F_{min}^o$

✓ SNIM technique is not applicable for W , ω , and P_D

where $\text{Re}[Z_{opt}]$ becomes greater than $\text{Re}[Z_{in}]$

for the maximum value of L_s ($L_{s,max}$) where F_{min} of the

LNA is not degraded

✓ $L_{s,max}$ can be identified by monitoring F_{min} vs. L_s

✓ There exists an optimum W that provides minimum

$\text{NF} (> F_{min}^o) \rightarrow$ Power-Constrained Noise Optimization Technique

3.3. Power Constrained Noise Optimization Technique

- ✓ Under fixed drain current, there exist a transistor size where the NF become minimum [Shaeffer].

$$W_{opt} \approx \frac{1}{3\omega C_{ox} R_s Q_{in,opt}} \quad (3.21)$$

$$Q_{in,opt} = |c| \sqrt{\frac{5\gamma}{\delta}} \left[1 + \sqrt{1 + \frac{3}{|c|^2} \left(1 + \frac{\delta}{5\gamma} \right)} \right] \quad (3.22)$$

- ✓ The minimum NF of this case is given by

$$F_{minP} \approx 1 + 2.4 \frac{\gamma}{\alpha} \left[\frac{\omega}{\omega_T} \right] \quad (3.23)$$

- ✓ Compare to Eq. (12), F_{minP} is higher than F_{min} .

$$F_{minP} \approx 1 + 2.4 \frac{\gamma}{\alpha} \left[\frac{\omega}{\omega_T} \right]$$

$$F_{min} = F_{min}^o = 1 + \frac{2}{\sqrt{5}} \frac{\omega}{\omega_T} \sqrt{\gamma\delta(1-|c|^2)}$$

- ✓ The reason is mismatch between Z_s and Z_{opt} and/or higher of L_s leads to higher F_{min}
- ✓ PCNO technique will eventually converge to the SNIM technique as the power consumption increases (satisfy Eqs. (17), (18), and (20))

 


Fig. 3.3. The simulation of NF vs V_{GS} at various transistor size at 2 GHz based on 0.8 μ m CMOS

3.4. Power-Constrained Simultaneous Noise and Input Matching Technique


 


Fig. 3.4. (a) The schematic of cascode topology apply to adopt PCSNIM technique and (b) Small signal equivalent circuit

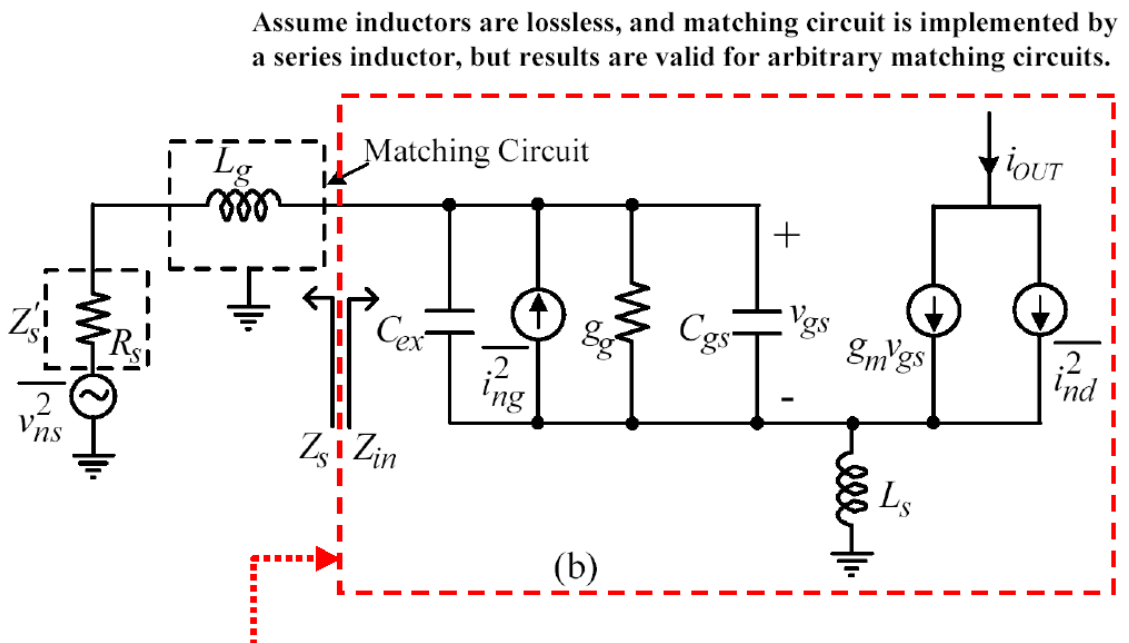

Obtain noise parameters by applying KCL/KVL

The noise parameters are given by [Appendix]

$$F = 1 + \frac{1}{g_m^2 R_s} \cdot \left\{ \gamma g_{d0} \cdot \left\{ \begin{aligned} &\left[1 + sC_t(sL_g + sL_s) \left(1 + |c| \alpha \sqrt{\frac{\delta_{eff}}{5\gamma}} \right) \right]^2 \\ &-(sC_t R_s)^2 \left(1 + |c| \alpha \sqrt{\frac{\delta_{eff}}{5\gamma}} \right)^2 \\ &-\frac{\alpha \delta_{eff}}{5} (1 - |c|^2) g_m (sC_t)^2 (R_s^2 - sL_g^2) \end{aligned} \right\} \right\} \quad (3.25)$$

✓ The mean-square gate-induce noise now is given by

$$\overline{i_{ng}^2} = 4kT \delta_{eff} \frac{\omega^2 C_t^2}{5g_{d0}} \Delta f \quad (3.24)$$

where

$$\delta_{eff} = \delta \cdot (C_{gs}^2 / C_t^2)$$

$$C_t = C_{gs} + C_{ex}$$

✓ Apply the same derivation method as SNIM technique
(See Appendix) → The noise parameters are given by

✓ **Noise Resistance**

$$R_n = \frac{\gamma}{\alpha} \cdot \frac{1}{g_m} \quad (3.26)$$

✓ **Minimum Noise Figure**

$$\begin{aligned} F_{min} &= 1 + \frac{2}{\sqrt{5}} \frac{\omega}{\omega_{T,eff}} \sqrt{\gamma \delta_{eff} (1 - |c|^2)} \\ &= 1 + \frac{2}{\sqrt{5}} \frac{\omega}{\omega_T} \sqrt{\gamma \delta (1 - |c|^2)} \end{aligned} \quad (3.27)$$

$$\omega_{T,eff} = g_m / (C_{gs} + C_{ex})$$

Same as those of the
CNM and SNIM
techniques



✓ **Optimum Noise Impedance**

$$Z_{opt} = \frac{\alpha \sqrt{\frac{\delta}{5\gamma(1-|c|^2)}} + j \left(\frac{C_t}{C_{gs}} + \alpha |c| \sqrt{\frac{\delta}{5\gamma}} \right)}{\omega C_{gs} \left\{ \frac{\alpha^2 \delta}{5\gamma(1-|c|^2)} + \left(\frac{C_t}{C_{gs}} + \alpha |c| \sqrt{\frac{\delta}{5\gamma}} \right)^2 \right\}} - sL_s \quad (3.28)$$

✓ **From Fig. 4 (b), the input impedance is given by**

$$Z_{in} = sL_s + \frac{1}{sC_t} + \frac{g_m L_s}{C_t} \quad (3.29)$$

The condition for the simultaneous noise and input matching

$$Z_{opt} = Z_{in}^* \begin{cases} \rightarrow \text{Re}[Z_{opt}] = \text{Re}[Z_s] & \text{Im}[Z_{in}] = -\text{Im}[Z_s] \\ \rightarrow \text{Im}[Z_{opt}] = \text{Im}[Z_s] & \text{Re}[Z_{in}] = \text{Re}[Z_s] \end{cases}$$



Re-express based
on Eqs. (3.26)-(3.28)

$$\frac{\alpha \sqrt{\frac{\delta}{5\gamma(1-|c|^2)}}}{\omega C_{gs} \left\{ \frac{\alpha^2 \delta}{5\gamma(1-|c|^2)} + \left(\frac{C_t}{C_{gs}} + \alpha |c| \sqrt{\frac{\delta}{5\gamma}} \right)^2 \right\}} = \text{Re}[Z_s] \quad (3.30)$$

$$\frac{j \left(\frac{C_t}{C_{gs}} + \alpha |c| \sqrt{\frac{\delta}{5\gamma}} \right)}{\omega C_{gs} \left\{ \frac{\alpha^2 \delta}{5\gamma(1-|c|^2)} + \left(\frac{C_t}{C_{gs}} + \alpha |c| \sqrt{\frac{\delta}{5\gamma}} \right)^2 \right\}} - sL_s = \text{Im}[Z_s] \quad (3.31)$$

$$sL_s + \frac{1}{sC_t} = -\text{Im}[Z_s] \quad (3.32)$$

$$\frac{g_m L_s}{C_t} = \text{Re}[Z_s] \quad (3.33)$$

✓ Like SNIM technique, Eq. (3.31) ~ Eq. (3.32) \rightarrow Eq. (3.32) can be dropped (for advanced technologies)

✓ The design parameters that can satisfy Eqs. (3.30), (3.31), (3.33) are V_{GS} , W , L_s , and C_{ex}

\rightarrow Eqs. (3.30), (3.31), (3.33) can be solved when power dissipation is fixed since three equations are provided by four unknowns

\rightarrow the simultaneous noise and input matching can be achieved at any level of power dissipation

Step-by-Step Design process


- 1) For a given P_D (power dissipation),
- 2) Choose V_{GS} from F_{min} vs. V_{GS} curve for an arbitrary transistor size (choose optimum F_{min})
- 3) Choose C_{gs} (or W) to satisfy $P_D \rightarrow$ determines $\text{Re}[Z_{opt}]$
- 4) Choose C_{ex} and L_s to satisfy $\text{Re}[Z_{in}] = \text{Re}[Z_{opt}]$
- 5) Given L_s satisfies $\text{Im}[Z_{in}^*] \approx \text{Im}[Z_{opt}]$ automatically
- 6) $\rightarrow Z_{opt} = Z_{in}^*$
- 7) Insert matching circuit to make $Z_{opt} = Z_{in}^* = Z_s$
- 8) Noise/input matched simultaneously at given P_D

1) Power Constrained

- Assume that we design LNA consuming 1 mW under supply voltage of 1.8 V.

1.1) Setup Environment

Draw Circuit as below

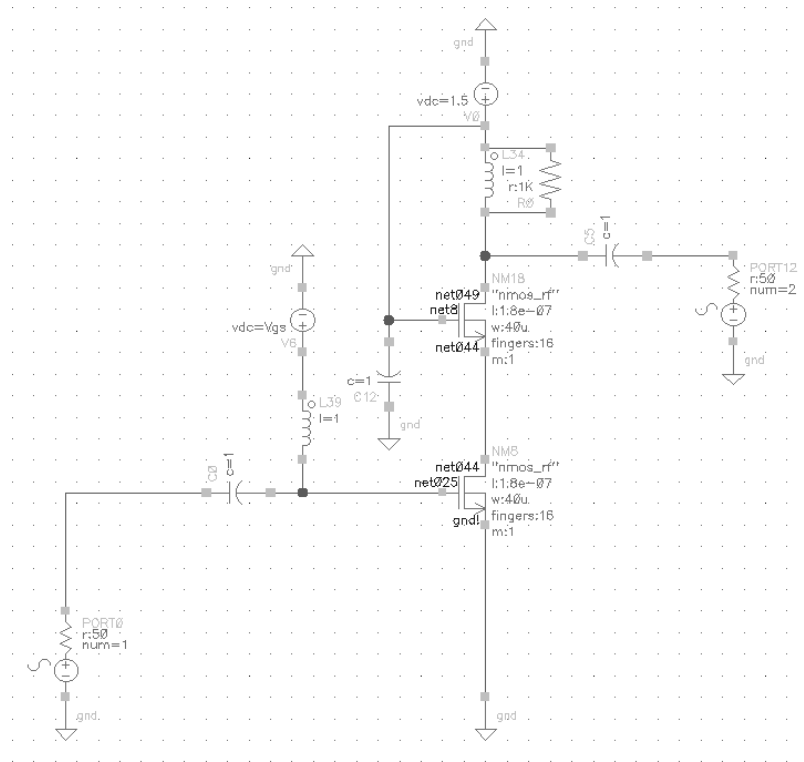

- Modify *Input Port* and *Output Port* as follows


Input Port

Output Port


Edit Object Properties			
OK Cancel Apply Defaults Previous Next Help			
Apply To <input type="checkbox"/> only current <input checked="" type="checkbox"/> instance			
Show <input type="checkbox"/> system <input checked="" type="checkbox"/> user <input type="checkbox"/> CDF			
Browse		Reset Instance Labels Display	
Property	Value	Display	
Library Name	analogLib	<input type="checkbox"/> off	
Cell Name	psir	<input type="checkbox"/> off	
View Name	symbol	<input type="checkbox"/> off	
Instance Name	PORT0	<input type="checkbox"/> off	
Add Delete Modify			
User Property	Master Value	Local Value	Display
lvignore	TRUE		<input type="checkbox"/> off
CDF Parameter		Value	Display
Frequency name	F1		<input type="checkbox"/> off
Second frequency name			<input type="checkbox"/> off
Noise file name			<input type="checkbox"/> off
Number of noise/freq pairs	0		<input type="checkbox"/> off
Resistance	50 Ohms		<input type="checkbox"/> off
Port number	1		<input type="checkbox"/> off
DC voltage			<input type="checkbox"/> off
Source type	sine		<input type="checkbox"/> off
Delay time			<input type="checkbox"/> off
Sine DC level			<input type="checkbox"/> off

Edit Object Properties			
OK Cancel Apply Defaults Previous Next Help			
Apply To <input type="checkbox"/> only current <input checked="" type="checkbox"/> instance			
Show <input type="checkbox"/> system <input checked="" type="checkbox"/> user <input type="checkbox"/> CDF			
Browse		Reset Instance Labels Display	
Property	Value	Display	
Library Name	analogLib	<input type="checkbox"/> off	
Cell Name	psir	<input type="checkbox"/> off	
View Name	symbol	<input type="checkbox"/> off	
Instance Name	PORT1	<input type="checkbox"/> off	
Add Delete Modify			
User Property	Master Value	Local Value	Display
lvignore	TRUE		<input type="checkbox"/> off
CDF Parameter		Value	Display
Frequency name	F0		<input type="checkbox"/> off
Second frequency name			<input type="checkbox"/> off
Noise file name			<input type="checkbox"/> off
Number of noise/freq pairs	0		<input type="checkbox"/> off
Resistance	50 Ohms		<input type="checkbox"/> off
Port number	2		<input type="checkbox"/> off
DC voltage			<input type="checkbox"/> off
Source type	sine		<input type="checkbox"/> off
Delay time			<input type="checkbox"/> off
Sine DC level			<input type="checkbox"/> off

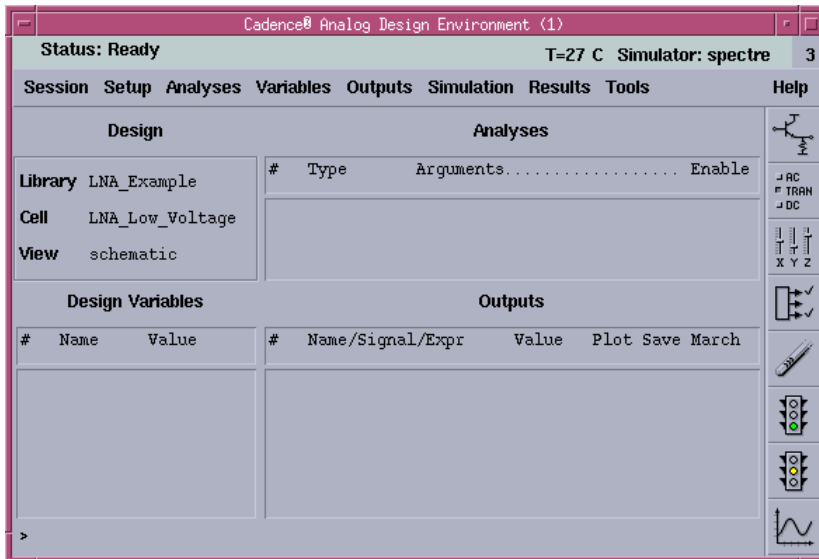- From the schematic window select: *Tool– Analog Environment*



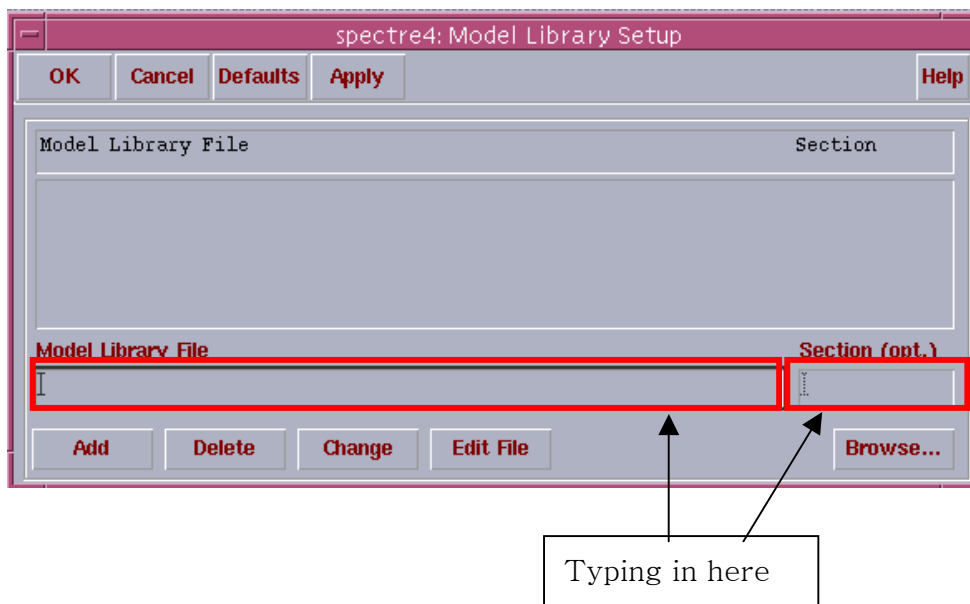- On the Analog Circuit Design Environment, Click *Setup–Model libraries*




➤ In the *Model Library File* and *Section* fields typing as follows

Model Library File	Section (opt.)
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_3v
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_na
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_3vna
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_m
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_3m
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	ees
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_bip
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	tt_bip3
/data1/RACS/DC_project/Tsmc18/models/mm018.scs	dio
/data1/RACS/DC_project/Tsmc18/models/rf018.scs	tt_rfmos
/data1/RACS/DC_project/Tsmc18/models/ResModel.scs	res_t


➤ You can Click **Browse** and go up to the directory, which contain the model library of the technology you would like to use. Or instructors will introduce the path of model library

- **Notice:** After you finish typing one section, press **Add** icon. If you make some mistakes, you can delete by click **Delete** icon
- On the Analog Environment Window, Click **Variable-Copy from cell view**.


- Analog Environment window looks like

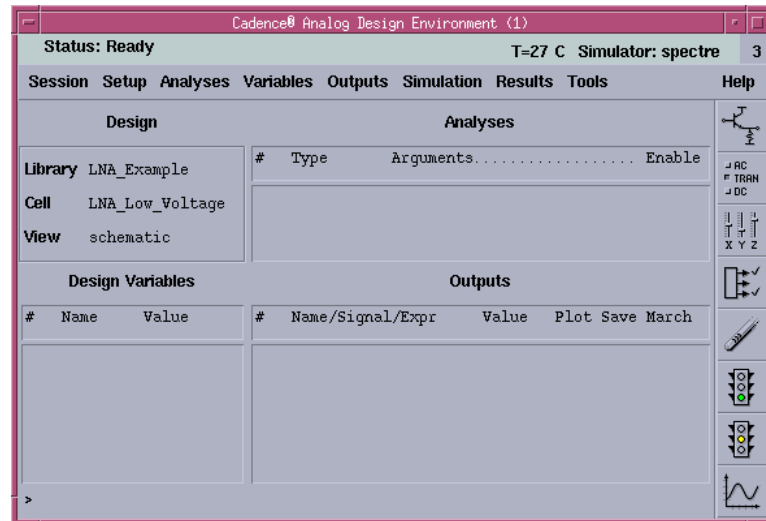

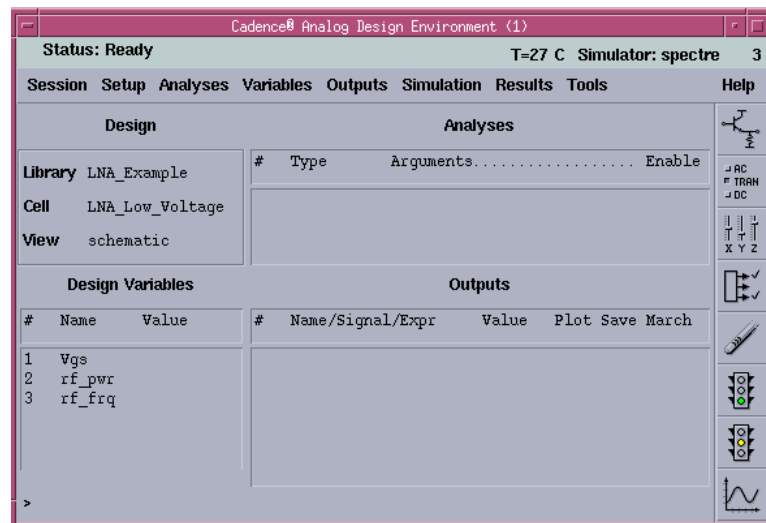- Choose *Variable* → *Copy From Cell View*, Analog Environment window becomes



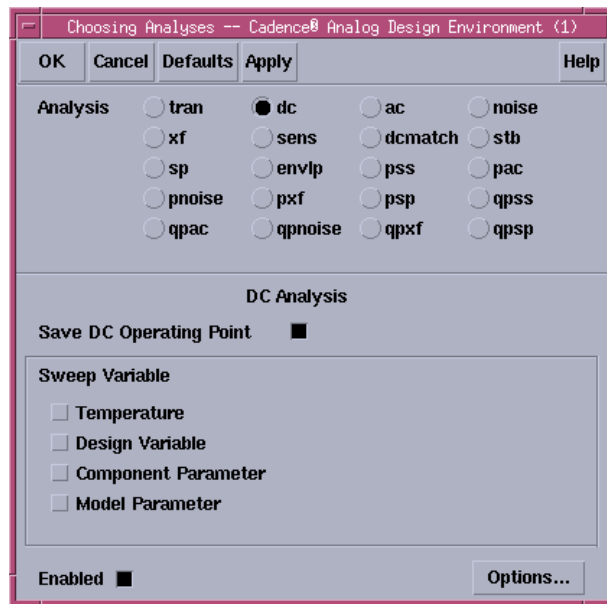- On the Analog Environment Window, Click *Analysis-Choose*, following window will appear



- Choose DC analysis
- Click on Save DC Operating Point
- Make sure that *Enable icon* is on

1.2. Run Simulation

- Click *Netlist and Run* icon



1.3. Plot Results

From Analog Design Environment Window, Click, *Results* → *Annotate* → *DC Node Voltage /DC Operating Points*

- Highline this additional capacitor and modify it as follows

Edit Object Properties

OK Cancel Apply Defaults Previous Next Help

Apply To: only current instance

Show: ☐ system ☒ user ☒ CDF

Browse Reset Instance Labels Display


Property	Value	Display
Library Name	analogLib	off
Cell Name	cap	off
View Name	symbol	off
Instance Name	C14	off

Add Delete Modify


CDF Parameter	Value	Display
Capacitance	Cex F	off
Initial condition		off
Model name		off
Width		off
Length		off
Multiplier		off
Scale factor		off
Temp rise from ambient		off
Temperature coefficient 1		off
Temperature coefficient 2		off


Typing in here

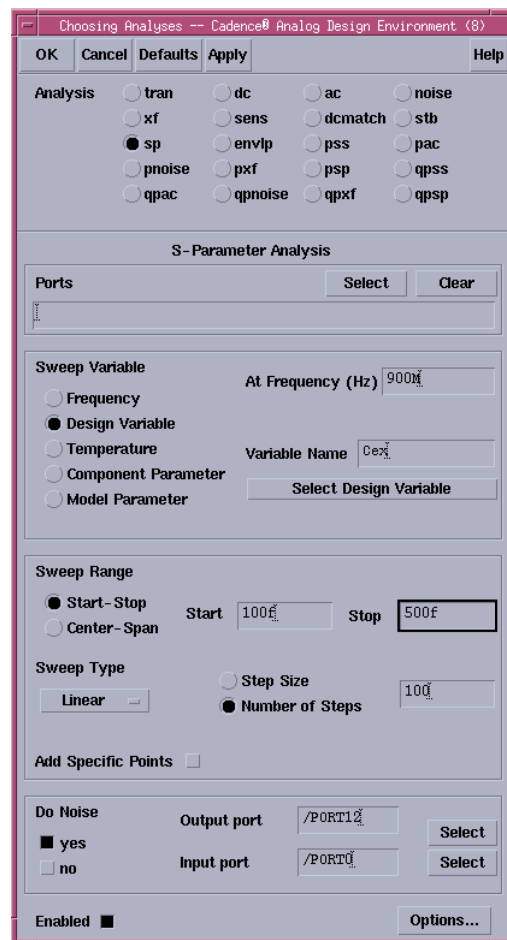- From Analog Design Environment, click Analysis → Choose, the Choosing Analyses window will appear, then modify it as follows



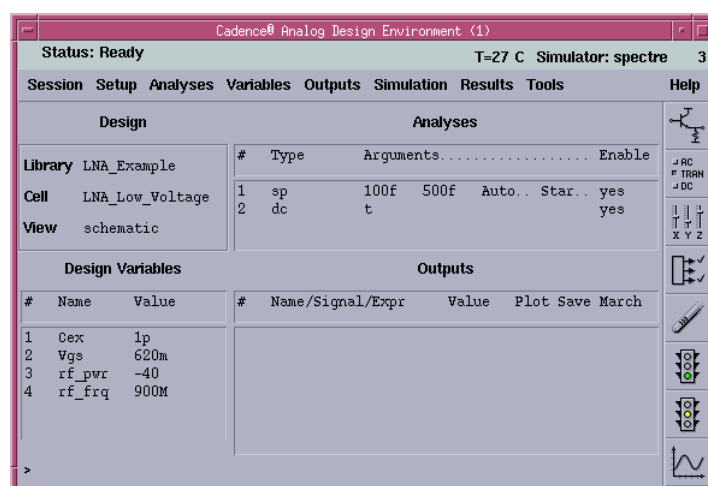
- Click **Apply** and **OK**, then the Analog Design Environment window becomes as follows



 

- From above Fig., we can choose the value of $C_{ex} = 210f$ in order to obtain the Real value of Γ_{opt} equal to 1.

Insert inductive degeneration

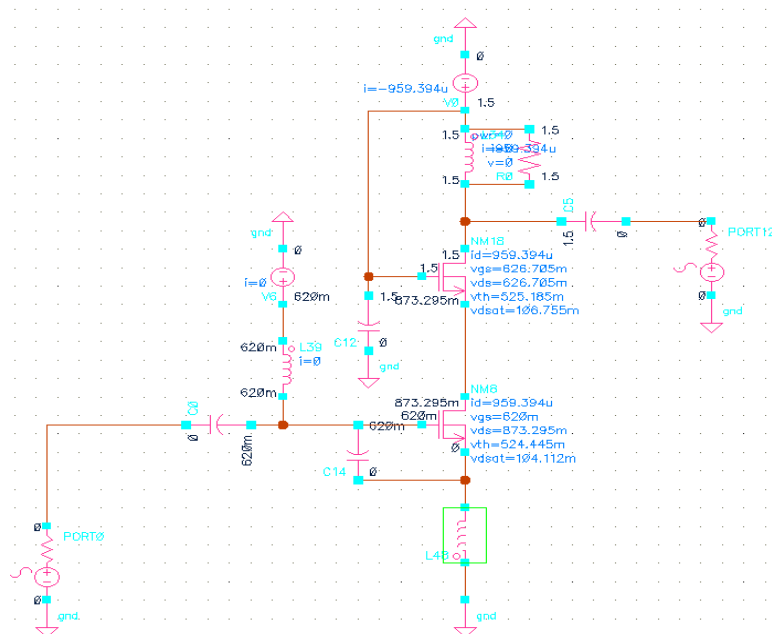

Choosing Analyses -- Cadence® Analog Design Environment (8)

OK Cancel Defaults Apply Help

Analysis ☐ tran ☐ dc ☐ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ stb
☒ sp ☐ envlp ☐ pss ☐ pac
☐ pnoise ☐ pxf ☐ psp ☐ qpss
☐ qpac ☐ qpnoise ☐ qpxf ☐ qpssp

S-Parameter Analysis

Ports

Sweep Variable At Frequency (Hz) 900M

☐ Frequency
☒ Design Variable
☐ Temperature Variable Name L_s
☐ Component Parameter
☐ Model Parameter

Sweep Range

☒ Start-Stop Start 0.4n Stop 4n
☐ Center-Span

Sweep Type


☐ Step Size 100
☒ Number of Steps

Add Specific Points ☐


Do Noise ☒ yes ☐ no

Output port /PORT12
Input port /PORT0

Enabled ☒

 


Zoom in

 

Choose $L_s = 1.4n$

Insert series gate inductor

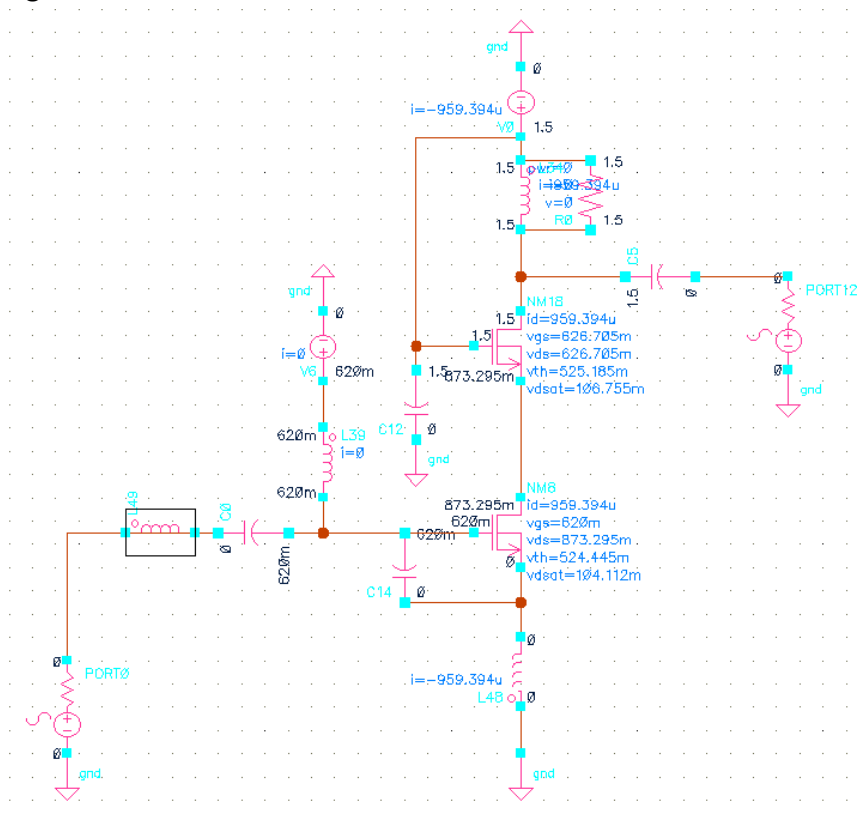

Edit Object Properties

OK Cancel Apply Defaults Previous Next Help

Apply To

Show ☐ system ☒ user ☒ CDF

Property	Value	Display
Library Name	analogLib	<input type="button" value="off"/>
Cell Name	ind	<input type="button" value="off"/>
View Name	symbol	<input type="button" value="off"/>
Instance Name	L49	<input type="button" value="off"/>

CDF Parameter	Value	Display
Inductance	<input type="text" value="1.4 H"/>	<input type="button" value="off"/>
Initial condition	<input type="text"/>	<input type="button" value="off"/>
Model name	<input type="text"/>	<input type="button" value="off"/>
Resistance	<input type="text"/>	<input type="button" value="off"/>
Multiplier	<input type="text"/>	<input type="button" value="off"/>
Temp rise from ambient	<input type="text"/>	<input type="button" value="off"/>

Choosing Analyses -- Cadence® Analog Design Environment (8)

OK Cancel Defaults Apply Help

Analysis ☐ tran ☐ dc ☐ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ stb
☒ sp ☐ envlp ☐ pss ☐ pac
☐ pnoise ☐ pxf ☐ psp ☐ qpss
☐ qpac ☐ qpnoise ☐ qpxf ☐ qpsp

S-Parameter Analysis

Ports Select Clear

Sweep Variable ☐ Frequency ☒ Design Variable ☐ Temperature ☐ Component Parameter ☐ Model Parameter

At Frequency (Hz) 900M

Variable Name Lg

Select Design Variable

Sweep Range ☒ Start-Stop ☐ Center-Span

Start 10n Stop 250n

Sweep Type ☒ Linear ☐ Step Size ☐ Number of Steps

100

Add Specific Points ☐

Do Noise ☒ yes ☐ no

Output port /PORT12 Select

Input port /PORT0 Select

Enabled ☒ Options...

Cadence® Analog Design Environment (1)


Status: Ready T=27 C Simulator: spectre 3

Session Setup Analyses Variables Outputs Simulation Results Tools Help


Design			Analyses			
Library	Cell	View	#	Type	Arguments.....	Enable
LNA_Example	LNA_Low_Voltage	schematic	1	sp	400p 4n Auto.. Star..	yes
			2	dc	t	yes

Design Variables			Outputs			
#	Name	Value	#	Name/Signal/Expr	Value	Plot Save March
1	Lg	1n				
2	Lo	1.4n				
3	Cex	210f				
4	Vgs	620m				
5	rf_pwr	-40				
6	rf_freq	900M				
 
> Results in /user2/NTkien/simulation/LNA_Low_Voltage/spectre/schematic



Choose $L_g = 107 \text{ nH}$

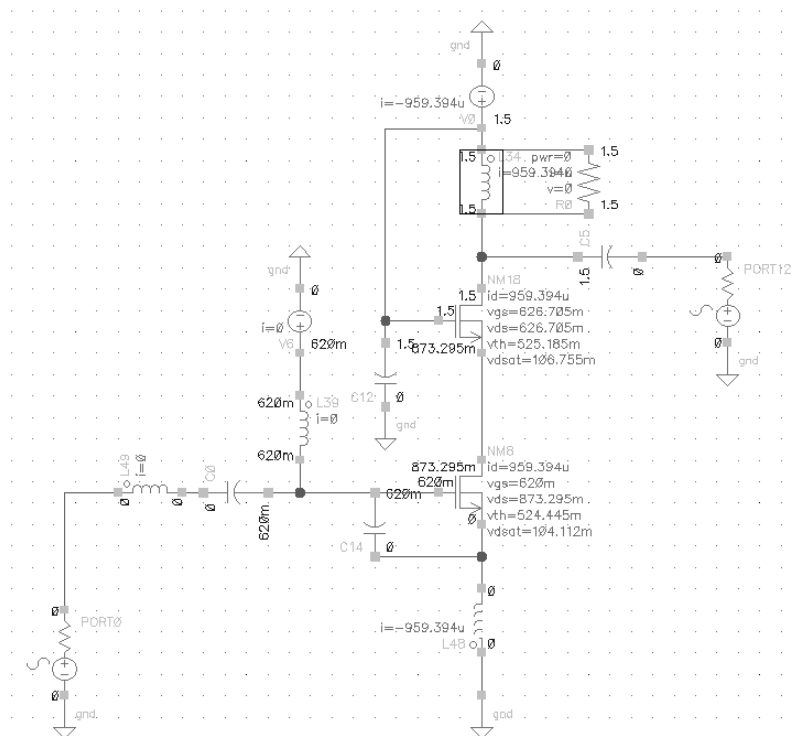

Highlight the output inductor and typing in the inductance field as L1

Edit Object Properties


OK Cancel Apply Defaults Previous Next Help

Apply To


Show ☐ system ☒ user ☐ CDF

Property	Value	Display
Library Name	analogLib	off
Cell Name	ind	off
View Name	symbol	off
Instance Name	L34	off


CDF Parameter	Value	Display
Inductance	L1 H	off
Initial condition		off
Model name		off
Resistance		off
Multiplier		off
Temp rise from ambient		off

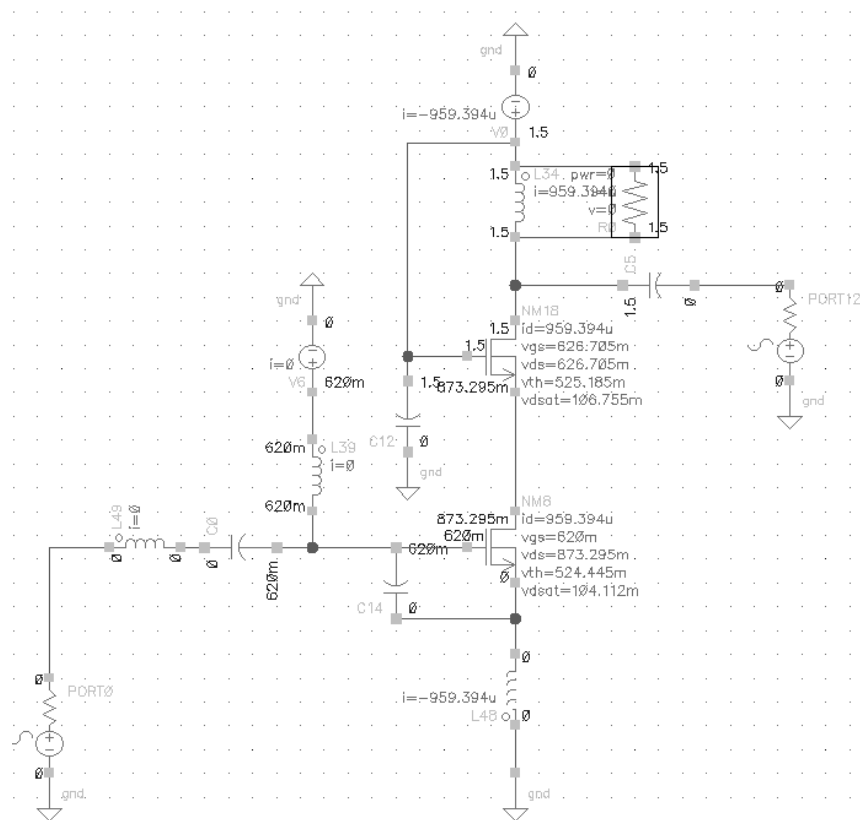

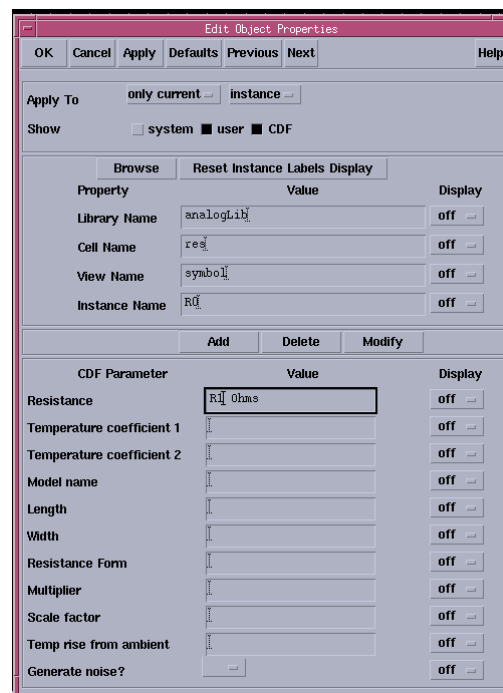Highlight the output resistor and typing in the resistance field as L1



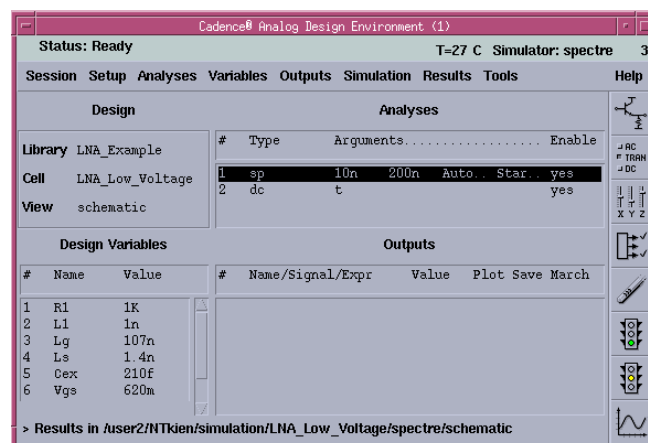- On the Analog Design Environment, click Variable → Copy from cell view, and then typing the primary value of L1 and R1 (any value).
- The Analog Design Environment window becomes



Parametric Analysis - spectre(7): LNA_Example LNA_Low_Voltage schematic

Tool Setup Analysis Help 83

Sweep 1

Variable Name

Add Specification


Range Type


From To

Step Control

Total Steps


Select ☐

 

 

Choose $R1 = 400 \text{ ohm}$, $L1 = 26 \text{ nH}$

Highline output capacitance

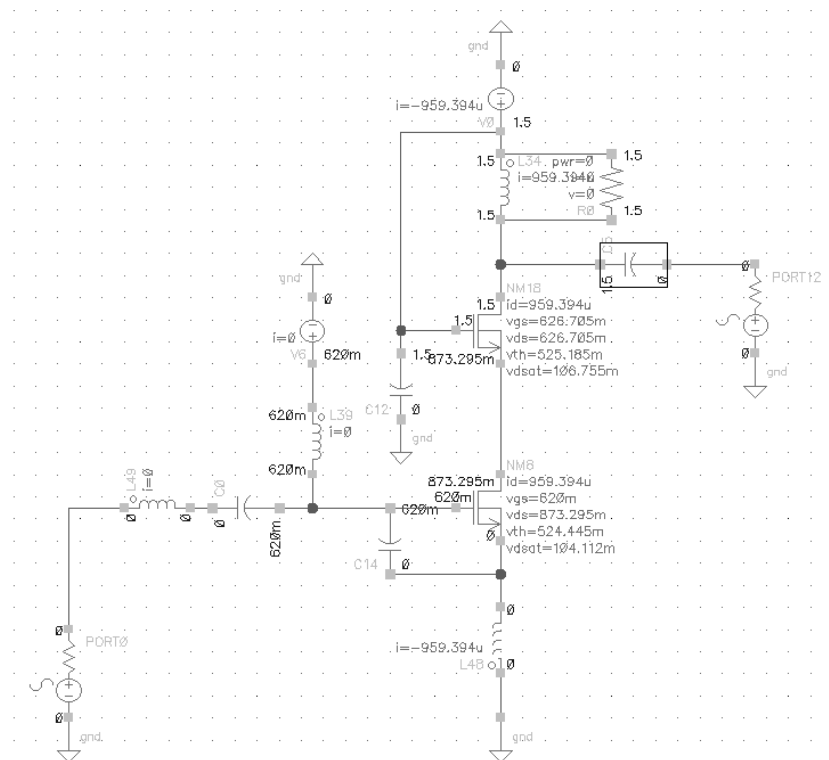

Edit Object Properties

OK Cancel Apply Defaults Previous Next Help

Apply To ☐ only current ☐ instance

Show ☐ system ☒ user ☐ CDF

Browse Reset Instance Labels Display

Property	Value	Display
Library Name	analogLib	off
Cell Name	cap	off
View Name	symbol	off
Instance Name	C5	off

Add Delete Modify

CDF Parameter	Value	Display
Capacitance	C1 F	off
Initial condition		off
Model name		off
Width		off
Length		off
Multiplier		off
Scale factor		off
Temp rise from ambient		off
Temperature coefficient 1		off
Temperature coefficient 2		off

Choosing Analyses -- Cadence® Analog Design Environment (1)

OK Cancel Defaults Apply Help

Analysis ☐ tran ☐ dc ☐ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ stb
☒ sp ☐ envlp ☐ pss ☐ pac
☐ pnoise ☐ pxf ☐ psp ☐ qpss
☐ qpac ☐ qpnoise ☐ qpxf ☐ qpss

S-Parameter Analysis

Ports Select Clear

Sweep Variable At Frequency (Hz) 900M

☐ Frequency
☒ Design Variable
☐ Temperature
☐ Component Parameter
☐ Model Parameter

Variable Name C1 Select Design Variable

Sweep Range

☒ Start-Stop Start 500M Stop 2p
☐ Center-Span

Sweep Type
Automatic



Add Specific Points ☐

Do Noise ☒ yes ☐ no

Output port /PORT1 Select
Input port /PORT0 Select


Enabled ☒ Options...

Analog Design Environment becomes

 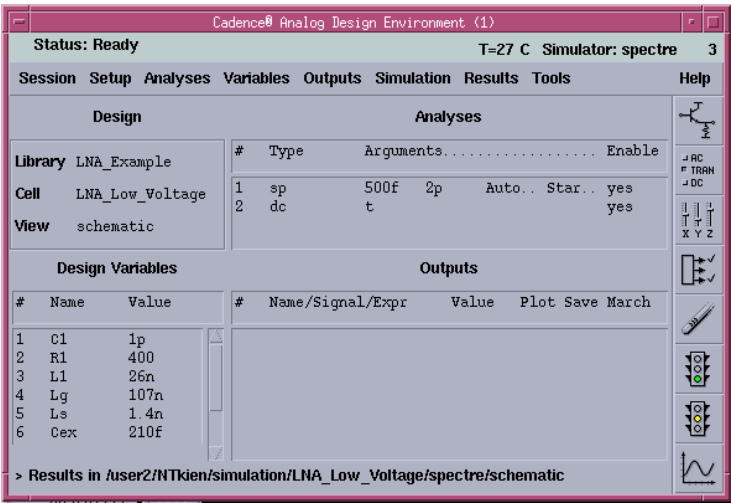




Choose C1 = 1.3 pF

Run S-Parmeters Simulation

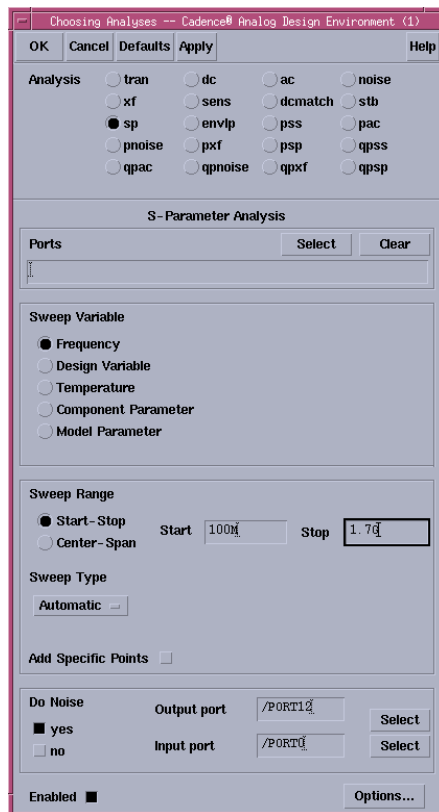


Analog Design Environment becomes

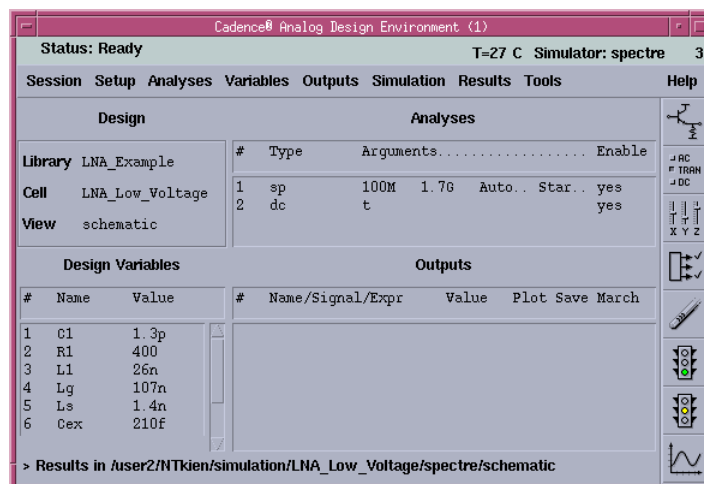

  



Stability factor

 



1. Image Rejection LNA

  1.1 Circuit Descriptions



Parasitic capacitance C_x degrades the noise performance.



  - Parallel resonance @ f_{sig} → improves noise figure



  - Series resonance @ f_{img} → improves image rejection




$$Z_f(s) = \frac{L_5 \cdot (C_3 + C_1) \cdot s^2 + 1}{C_1 \cdot C_3 \cdot L_5 \cdot s^3 + C_3 \cdot s}$$


$$\omega_p = 0$$

$$\omega_p = \pm \frac{1}{\sqrt{L_5 \cdot C_1}}$$

 
$$\omega_z = \pm \frac{1}{\sqrt{L_5 \cdot (C_3 + C_1)}}$$



Equivalent Noise Circuit for the LNA

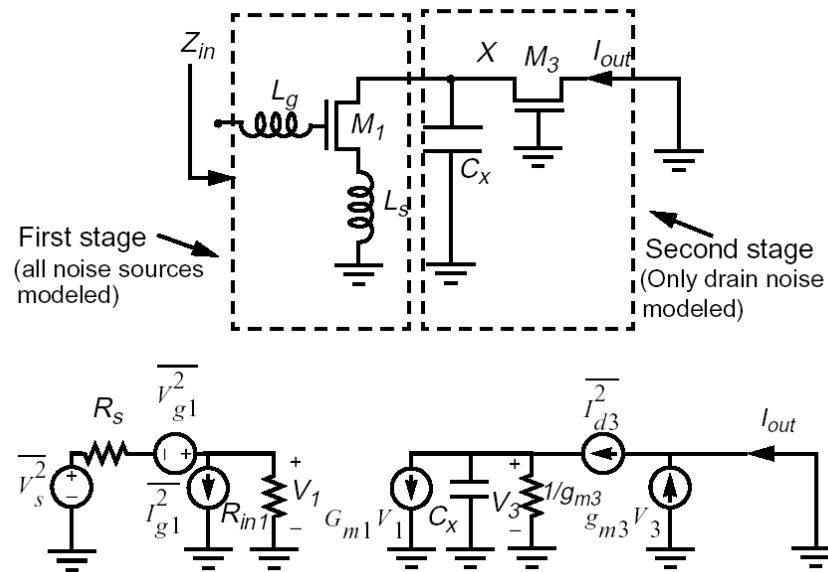

Filter Noise Model

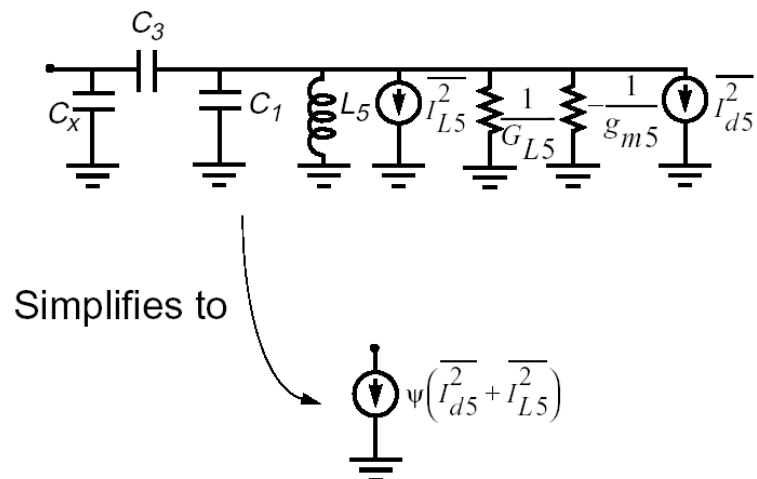

Noise Formulas

$$F_{no-filter} = F_1 + 4R_s \gamma_3 g_{do3} \left(\frac{\omega_0^2}{\omega_T^2} \right) \left(\frac{C_x^2}{g_{m3}^2} \omega_0^2 \right)$$

- Overall NF of LNA/Filter is

$$F_{tot} = F_1 + \psi \cdot 4R_s (\gamma_5 g_{do5} + G_{L5}) \left(\frac{\omega_0^2}{\omega_T^2} \right)$$

$$\text{Where } \psi = \frac{C_3^2 \cdot \omega_0^2}{\left(\frac{C_3^2}{C_x + C_3} \right)^2 \cdot \omega_0^2 + (G_{L5} - g_{m5})^2},$$

$$F_1 = 1 + \frac{1}{g_m^2 R_s} \cdot \left\{ \begin{array}{l} \gamma g_{d0} \cdot \left\{ \left[1 + s^2 C_{gs} (L_g + L_s) \left(1 + /c / \alpha \sqrt{\frac{\delta}{5\gamma}} \right) \right]^2 \right\} \\ - (s C_{gs} R_s)^2 \left(1 + /c / \alpha \sqrt{\frac{\delta}{5\gamma}} \right)^2 \\ - \frac{\alpha \delta}{5} (1 - /c /)^2 g_m (s C_{gs})^2 (R_s^2 - s L_g^2) \end{array} \right\}$$

- Note that the impedance of the filter at the frequency of the pole is high enough $\rightarrow F_{total} = F_1$


1.2 Circuit Implementation

1.2.1 Setup Environment


Assume that we design the image rejection LNA operating at 5 GHz with the image signal equal to 5.5 GHz → Based on Eq. We can calculate the value of each component of the image rejection circuit as follows:

$L1$ (image rejection filter) = 2.2 nH, $C1$ (Image Rejection Filter) = 100f, $C3$ (Image Rejection Filter) = 300f


Build the circuit as follows

 

 
- The model of bond-wire is shown in below



 - The model of bond pad power is shown in below



 - The model of bond pad shield is shown in below



Size of bias transistor

Edit Object Properties

OK Cancel Apply Defaults Previous Next Help

Apply To:

Show: ☐ system ☒ user ☐ CDF

Property	Value	Display
Library Name	tsmc18rf	off
Cell Name	rnmos2v	off
View Name	symbol	off
Instance Name	NM0	off

CDF Parameter	Value	Display
Model name	nch	off
I (M)	180.0n A	off
w (M)	2u M	off
Number of Fingers	1	off
Width Per Finger	2u M	off
multiplier	2	off
Calc Diff Params	<input checked="" type="checkbox"/>	off
Source diffusion area	9.6e-13	off
Drain diffusion area	9.6e-13	off
Source diffusion periphery	4.96u M	off
Drain diffusion periphery	4.96u M	off

The way to find the value of input and output matching are the same as the Low Noise Amplifier 1: Theory. However, the step to determine the value of L_s is different because now the degeneration inductor is made by bonding wire instead of using onchip inductor.

Edit Object Properties

OK Cancel Apply Defaults Previous Next Help

Apply To:


Show: ☐ system ☒ user ☐ CDF

Property	Value	Display
Library Name	LNA_Example	off
Cell Name	b_wire	off
View Name	symbol	off
Instance Name	I34	value

User Property	Master Value	Local Value	Display
interfaceLastC..	3 20:54:18 2002		off
partName	b_wire		off
vendorName			off

CDF Parameter	Value	Display
length	L_s	off

Sweep the value of L_s

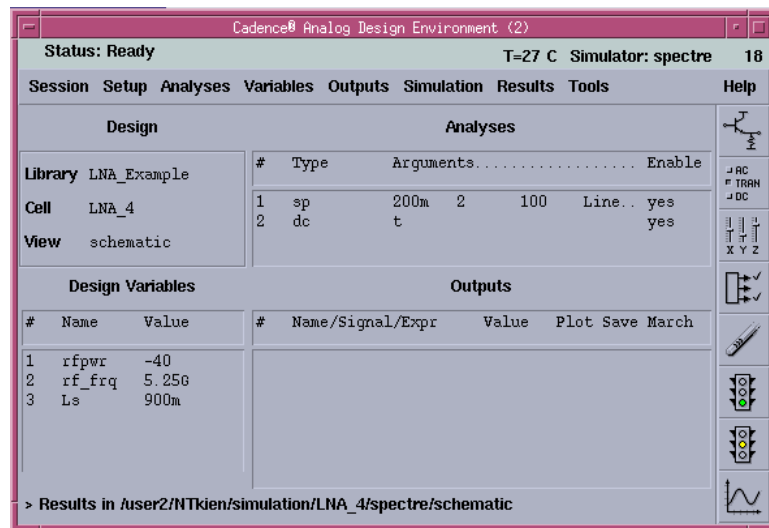


Finally, we obtain the value of each component as follows

$L_s = 0.3\text{m}$, $L_g = 2.5\text{ nH}$, L_d (output inductance) = 2.3 nH , R_d (Output resistance) = 250 ohm


C_d (Output capacitance) = 1443 fF

1.2.2 Run S-parameters simulation

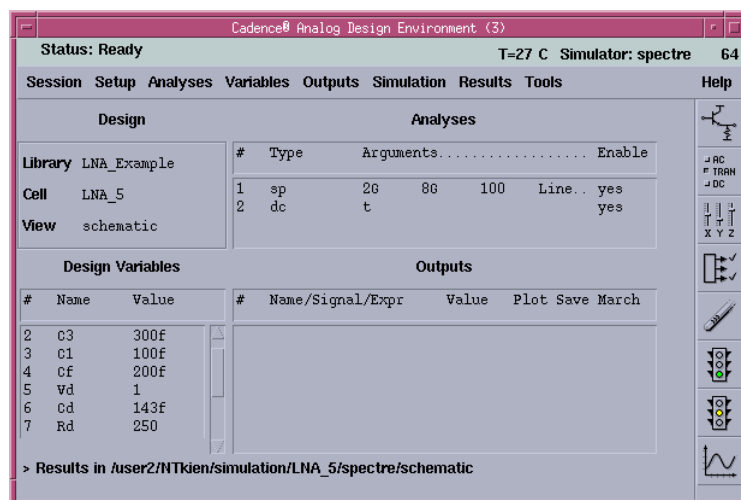


1.2.3 Plot Results


1) S-Parameters

 

2) NF and NFmin

 


1.2.4. Check Linearity

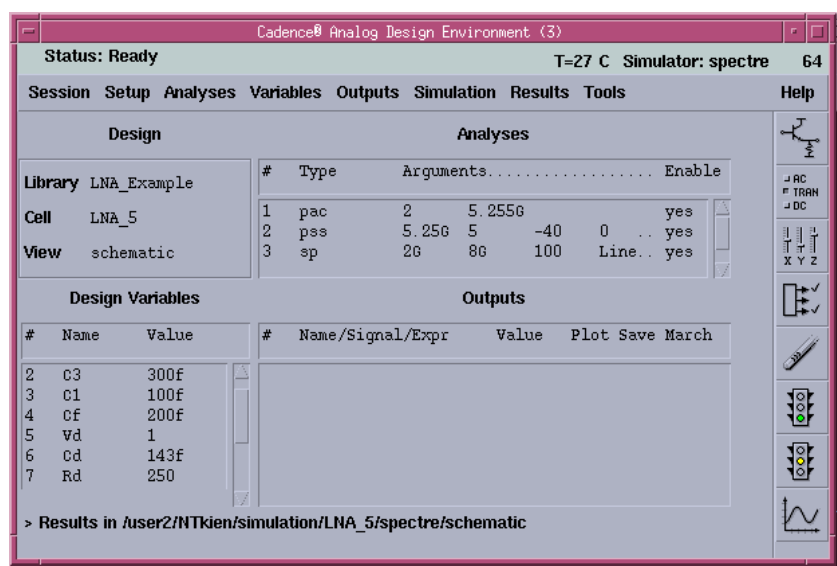


1.2.5. Plot Results

1) 1dB compression point

 


2) IIP3

 

2. Gain Enhancement Technique Using Positive Feedback

2.2.1 Circuit Descriptions

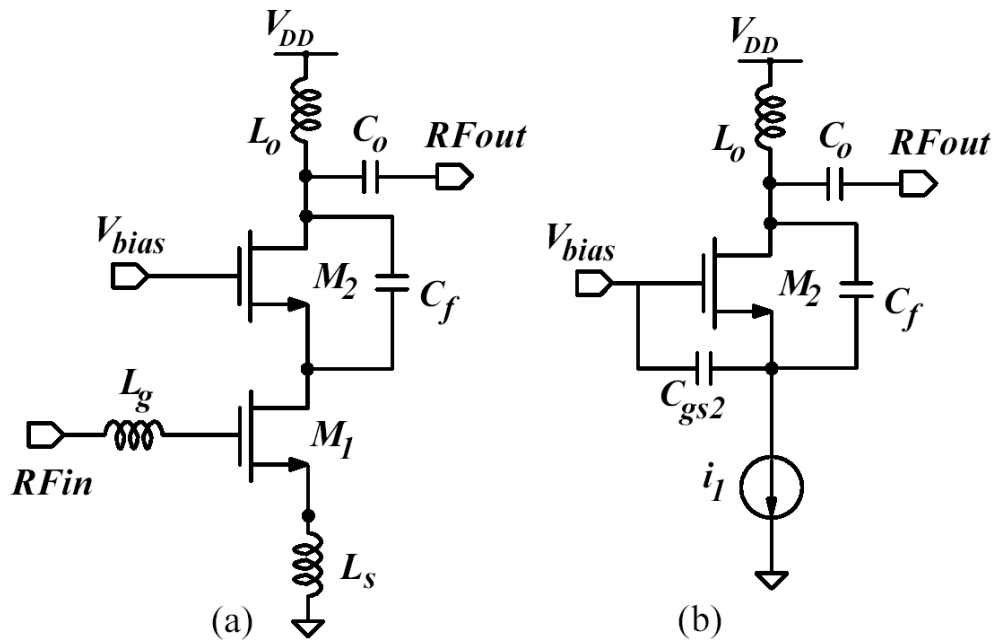

- The positive feedback is realized by C_f
- This phenomenon can be understood by another point of view as the form of oscillator. C_{gs1} , C_f , and M_1 constitute an oscillator topology with inductive termination at the output.
- The gain of amplifier without C_f is given by

$$A_v = g_{m1} Q_{in} \frac{1}{G_{tot}} = G_{eff} \frac{1}{G_{tot}} \quad (5.1)$$

- g_m is the transconductance of M_1 ,
- Q_{in} is the quality factor of the input circuit
- G_{eff} is the effective transconductance of the amplifier
- G_{tot} is the total transconductance at the drain of M_2 and is dominated by the equivalent parallel conductance of the inductor (G_P).

$$G_P = \frac{1}{Q_L^2 R_{L_o}} \quad (5.2)$$

- R_{L_o} is the series resistance of the inductor
- Low Q_L lead to high $G_P \rightarrow$ high $G_{tot} \rightarrow$ Limit the A_v of the amplifier
- From (5.1) \rightarrow Gain of amplifier can be improved by larger G_{eff} or larger $L_o \rightarrow$ larger power consumption or an impracticably larger value for the inductor
- The Q of the amplifier without C_f is given by

$$Q = \frac{1}{G_{tot}} \sqrt{\frac{C_{tot}}{L_o}} \quad (5.3)$$

- C_{tot} is the total capacitance at the drain of M_2 .
- From (5.2) and (5.3): Low Q_L will also limit the Q of amplifier
- Assume that $\omega \ll g_{m2} / (C_{gs2} + C_f)$, from Fig.-b, the negative conductance (G_N) is generated by C_f is

$$G_N = \frac{\omega^2 C_{gs2} (C_N + C_{gd2})}{g_{m2}} \quad (5.4)$$


- The total conductance now is given by

$$G_{tot} = G_P - G_N \quad (5.5)$$

- From (5.5) by using C_f , the total conductance is reduced → improve gain of LNA
- Note that no additional active is used therefore no more DC power dissipated and no noise contributed.
- The limit to amount of feedback is governed by stability consideration. To ensure the stability condition, G_{tot} must always positive.

2.2.2 Circuit Implementation



2.2.1 Setup Environment


 


The value of component of matching network: $L_s = 530 \text{ nH}$, $C_g = 2.6 \text{ pF}$

The value of output matching network: L_1 , R_1 va C_1 are:


2.2.2 Runsimulation

  

  


Insert additional capacitor connected to drain and source terminal of the cascode transistor

 
- Highline this capacitor and as set its capacitance as variable C_f



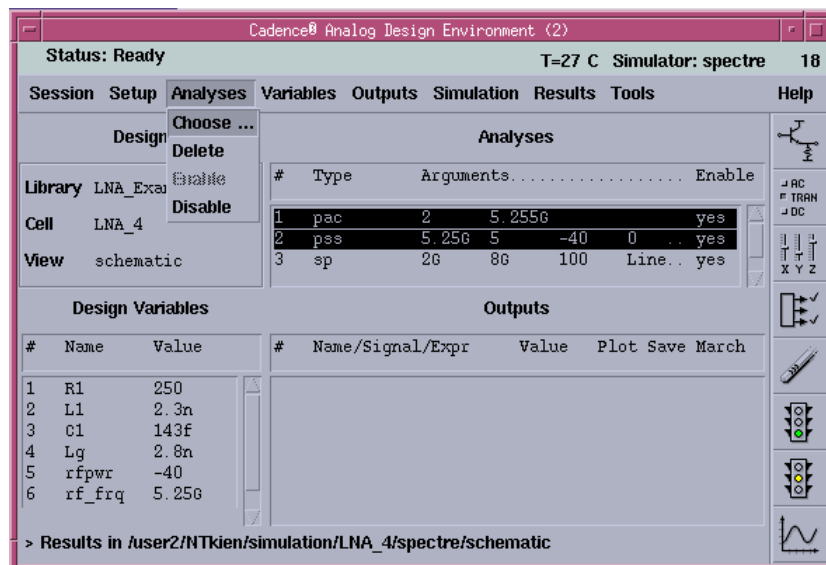
On the Analog Design Environment window, invisible PSS and PAC analyses by doing as follows



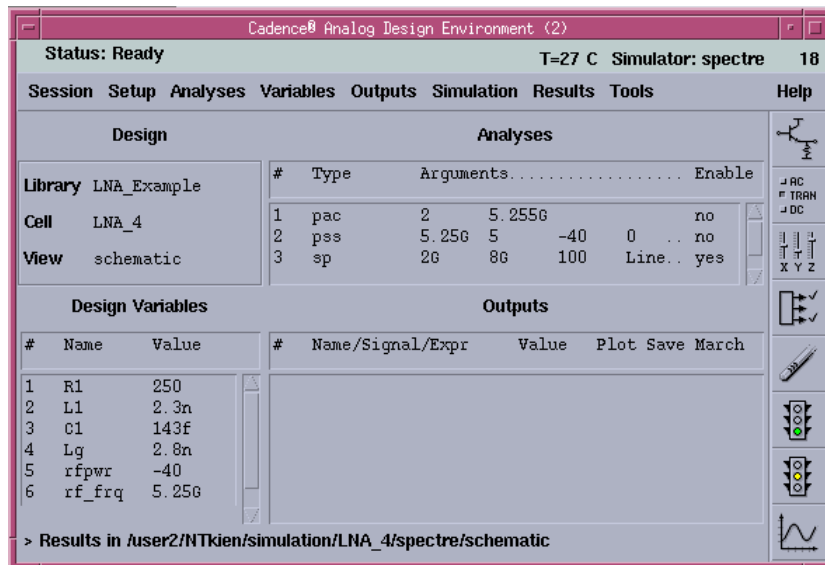
➤ Analog Design Environment window becomes




Click Variable → Copy from cell view

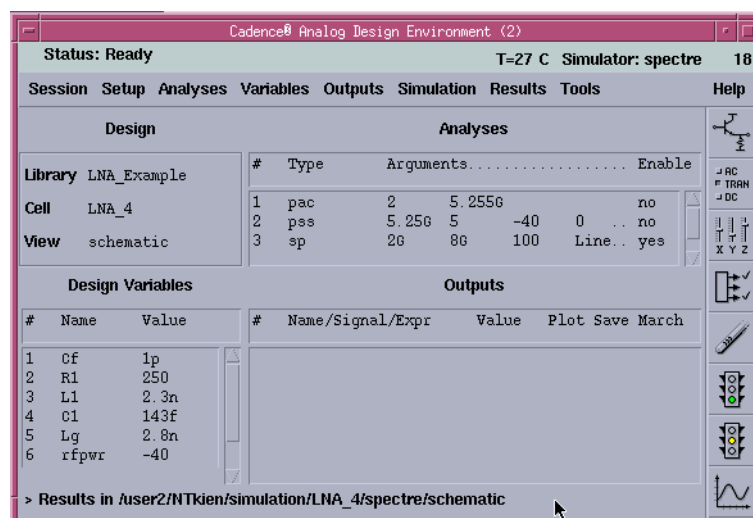

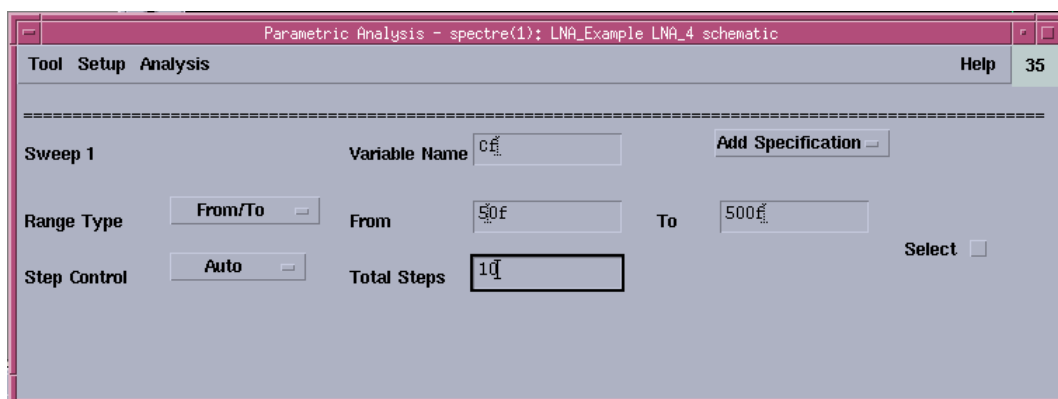
Click **tool** the Parametric Analysis window will appear. After that we modify it as follows



 Click Analysis → Start in order to run the simulation. After simulation, Plot S21, and K-factor we can obtain results as follows



K factor

 

Considering the value of K factor → choose value of Cf.